

1/100E02

# 國立臺北科技大學 110 學年度碩士班招生考試

系所組別：2401 光電工程系碩士班

## 第二節 電子學 試題 (選考)

第 1 頁 共 2 頁

### 注意事項：

1. 本試題共 5 題，共 100 分。
2. 不必抄題，作答時請將試題題號及答案依照順序寫在答案卷上。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

1. The circuit in Fig. 1 implements a complementary-output rectifier. Assume a 0.7-V drop across each conducting diode. If the magnitude of the average of each output is to be 15 V.
  - (a) Plot and label the waveform of  $v_o^+$  and  $v_o^-$  and (b) find the amplitude of the sine wave across the secondary winding  $v_s$  (c) What is the PIV of each diode?

(各小題配分: 10 分, 5 分, 5 分)

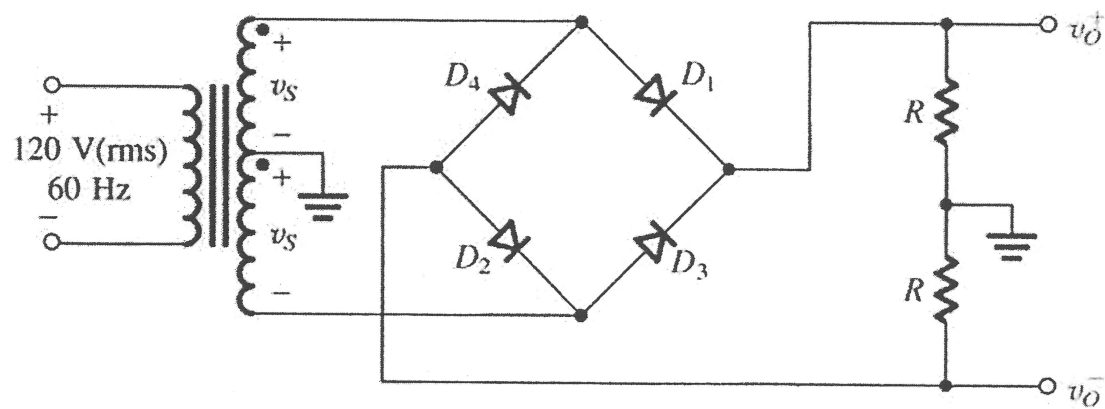


Fig. 1

2. A difference-amplifier circuit in Fig. 2 has  $R_1 = R_3 = 2 \text{ k}\Omega$  and  $R_2 = R_4 = 200 \text{ k}\Omega$ .
  - (a) Find the value of the differential gain  $A_d$ .
  - (b) Find the value of the differential input resistance  $R_{id}$  and the output resistance  $R_o$ .
  - (c) If the resistors have 1% tolerance (i.e., each can be within  $\pm 1\%$  of its nominal value), find the worst-case common-mode gain  $A_{cm}$  and the corresponding value of CMRR. (各小題配分: 5 分, 10 分, 5 分)

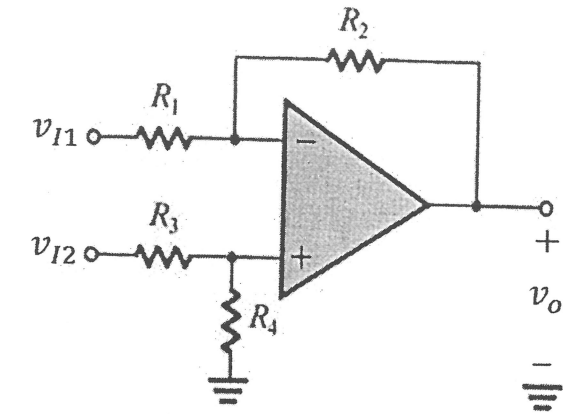


Fig. 2

3. The amplifier shown in Fig. 3 has  $R_{sig} = R_L = 1 \text{ k}\Omega$ ,  $R_C = 1 \text{ k}\Omega$ ,  $R_B = 47 \text{ k}\Omega$ ,  $\beta = 100$ ,  $C_\mu = 0.8 \text{ pF}$ , and the unity-gain frequency  $f_T = 600 \text{ MHz}$ .
  - (a) Find the dc collector current of the transistor.
  - (b) Neglecting  $r_o$ , find the midband voltage gain ( $v_o/v_b$ ) from base to collector (neglect the effect of  $R_B$ ).
  - (c) Use the gain obtained in (b) to find the input resistance  $R_{in}$  that arises as a result of  $R_B$ .
  - (d) Find the overall gain at midband ( $v_o/v_{sig}$ ).
  - (e) Find upper 3 dB frequency  $f_H$ . (每小題 5 分)

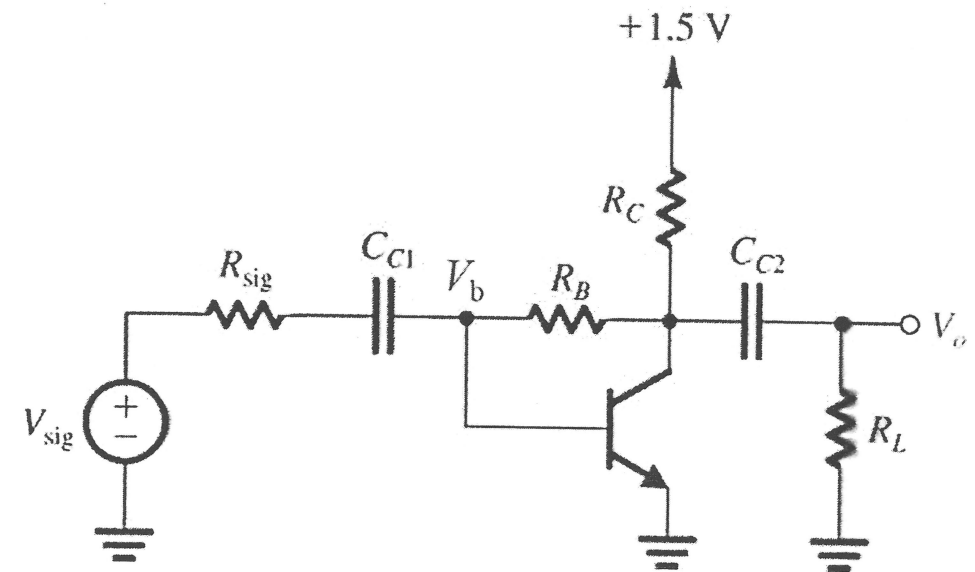


Fig. 3

注意：背面有試題

4. A CS amplifier circuit is shown in Fig. 4, where the NMOS transistor is biased to have  $g_m=1 \text{ mA/V}$  and  $r_o=100 \text{ k}\Omega$ . If  $C_{gs}=1 \text{ pF}$  and  $C_{gd}=0.2 \text{ pF}$ . Please find
- midband gain ( $v_o/v_{sig}$ )
  - input resistance connected to the source  $v_{sig}$
  - lower 3 dB frequency  $f_L$
  - upper 3 dB frequency  $f_H$ .
- (每小題 5 分)

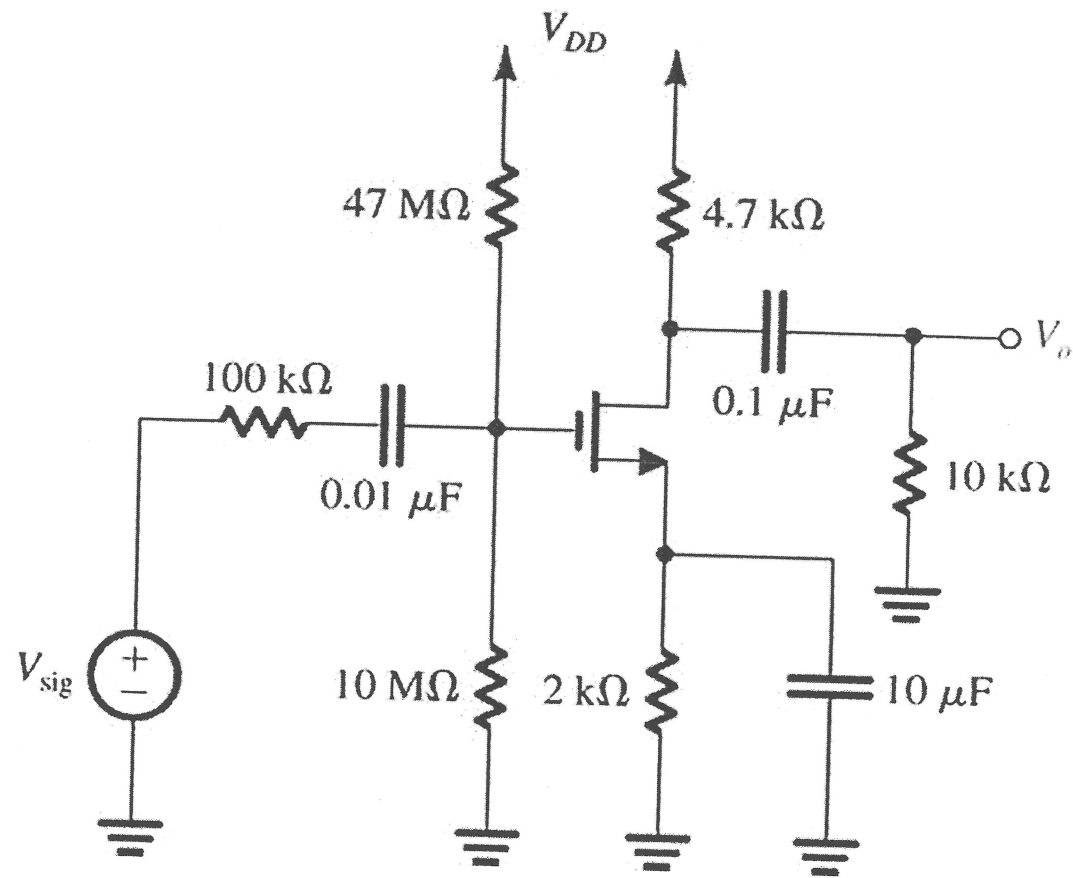


Fig. 4

5. Consider ideal diodes in the circuit of Fig. 5. Please plot and label the transfer characteristic curve of the circuit. (本題 15 分)

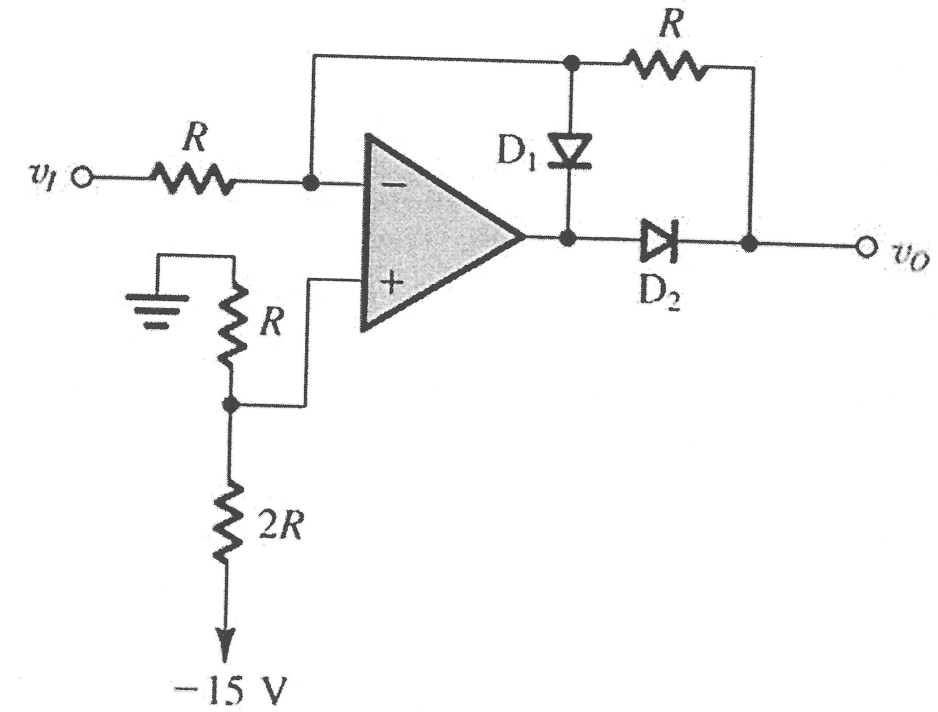


Fig. 5