

國立臺北科技大學 106 學年度碩士班招生考試

系所組別：1503 自動化科技研究所

第二節 電子學 試題 (選考)

第一頁 共二頁

注意事項：

1. 本試題共 5 題，共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

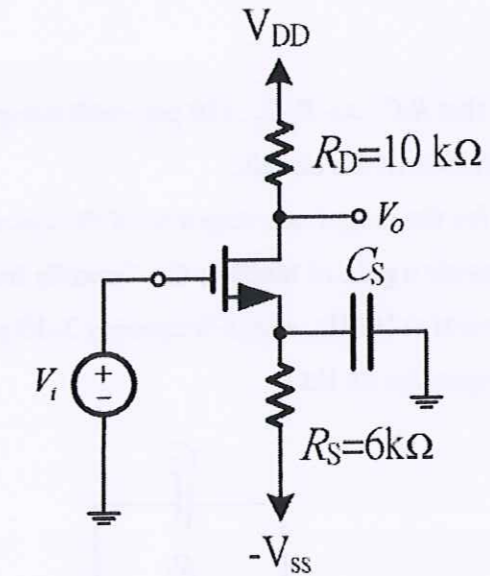


Figure 2

1. Figure 1 shows a circuit having an input resistance of 100 kΩ and a gain that can be varied from -1 V/V to -10 V/V using the 10-kΩ potentiometer R_4 . What is the voltage gain when the potentiometer is set exactly at its middle value? (15 pts)

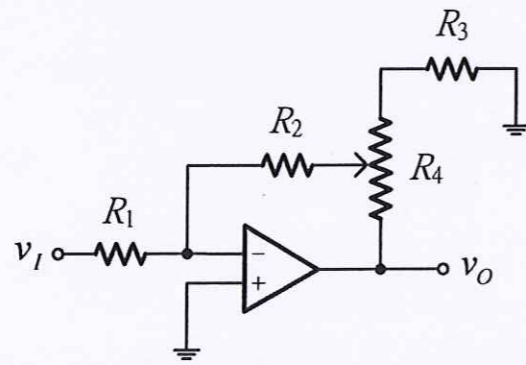


Figure 1

3. For each of the circuits shown in Figure 3, find the emitter, base, and collector voltages and currents. Use $\beta=30$, but assume $|V_{BE}|=0.7\text{ V}$ independent of current level. (20 pts, each sub-problem is 5pts)

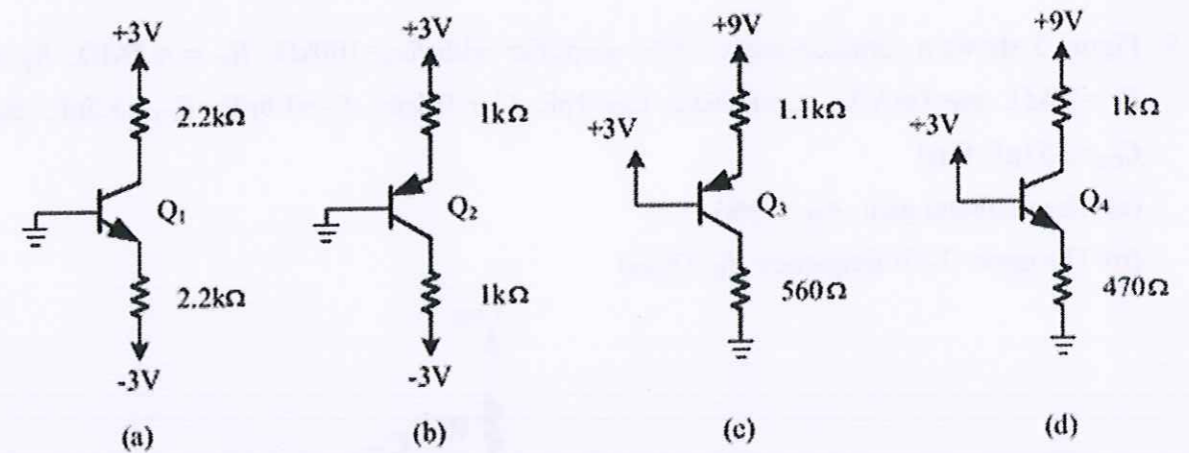


Figure 3

2. The amplifier shown in Fig. 2 is biased to operate at $I_D=1\text{mA}$, $g_m=1\text{ mA/V}$. Neglecting r_o . (20 pts, each sub-problem is 10 pts)
 - (a) Find the midband gain.
 - (b) Find the value of C_S that places f_l (the low 3-dB frequency) at 10Hz.

注意：背面尚有試題

4. See Figure 4 and assume that $R_1 C_1 \gg R_2 C_2$. (30 pts, each sub-problem is 10pts)
- Derive the transfer function of the circuit.
 - Sketch the Bode plot for the magnitude response of the circuit.
 - Design a circuit to provide a gain of 60dB in the "middle frequency range," a low-frequency 3-dB point at 100Hz, a high-frequency 3-dB point at 10kHz, and an input resistance (at high frequency) of 1k Ω .

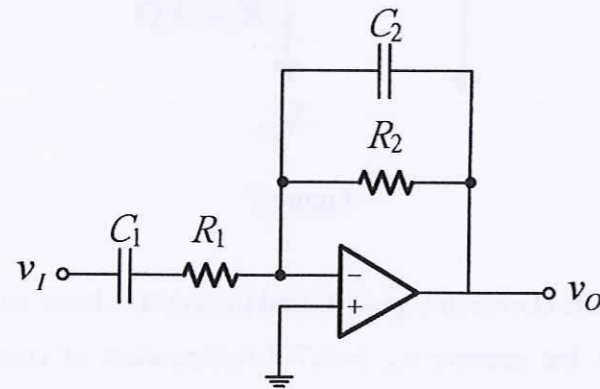


Figure 4

5. Figure 5 shows a common-source (CS) amplifier with $R_{sig}=100\text{k}\Omega$, $R_G = 4.7\text{M}\Omega$, $R_D = R_L = 15\text{k}\Omega$, $g_m=1\text{mA/V}$, $r_o=150\text{k}\Omega$, $C_{gs}=1\text{pF}$, $C_{gd}=0.4\text{pF}$, $C_S = 1.6\mu\text{F}$, $C_{C1} = 3.3\text{nF}$, and $C_{C2}=0.53\mu\text{F}$. Find
- The midband gain A_M . (7pts)
 - The upper 3-dB frequency f_H . (8pts)

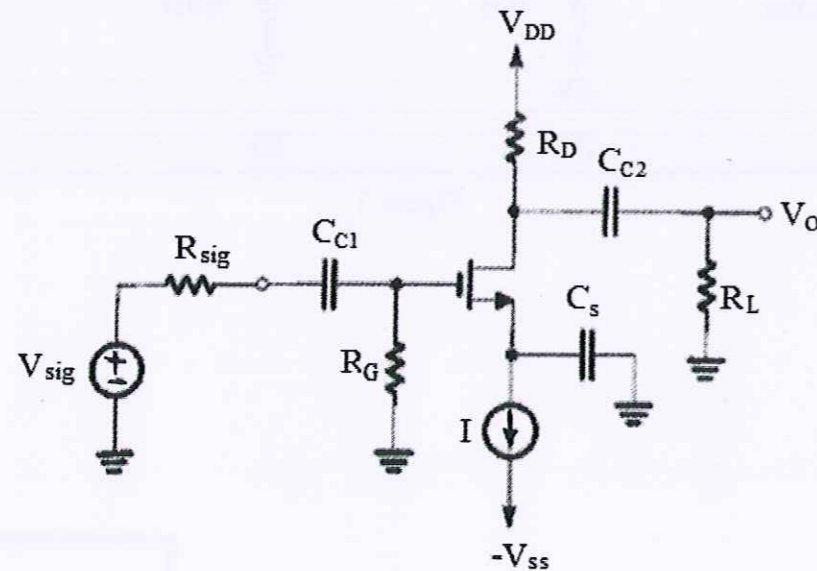


Figure 5