

# 國立臺北科技大學 111 學年度碩士班招生考試

系所組別：2152 電機工程系碩士班戊組

## 第一節 數位邏輯 試題 (選考)

第 1 頁 共 1 頁

### 注意事項：



1. 本試題共八題，共 100 分。
2. 不必抄題，作答時請將試題題號及答案依照順序寫在答案卷上。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

1. (10%) (a)  $A = 101010$  and  $B = 011101$  are 1's complement numbers. Perform  $A - B$  and indicate whether overflow occurs. (5%)  
(b) Repeat part (a) assuming the numbers are 2's complement numbers. (5%)
2. (15%) Simplify the following expressions to a minimum sum of products. Only individual variables should be complemented.  
(a)  $[(A' + B')' + (A'B'C)' + C'D]'$  (5%)  
(b)  $(a' + c + d)(a' + b + e)(a + c' + e')(c + d + e')(b + c + d' + e)(a' + b' + c + e')$  (10%)
3. (10%) Find a minimum two-level, multiple-output AND-OR gate circuit to realize these functions.  


$$f_1(a, b, c, d) = \sum m(2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$$

$$f_2(a, b, c, d) = \sum m(2, 3, 5, 6, 7, 10, 11, 14, 15)$$
  
$$f_3(a, b, c, d) = \sum m(6, 7, 8, 9, 13, 14, 15)$$
4. (5%) Draw the timing diagram for V and Z for the circuit. Assume that the AND gate has delay of 10 ns and the OR gate has a delay of 5 ns.



 5. (10%) Realize a full adder using a 3-to-8 line decoder with inverting outputs and two NAND gates.
6. (15%) The following circuit is intended to be a gated latch circuit where the signal G is the gate.  
(a) Derive the next-state equation for this circuit using Q as the state variable and P as an output. (10%)  
(b) Are there any restrictions on the allowable input combinations on M and N? Explain your answer. (5%)



7. (20%) Design a 3-bit counter which counts in the sequence:  
001, 011, 010, 110, 111, 101, 100, (repeat) 001, ...  
(a) Use D flip-flops. (10%)  
(b) Use T flip-flops. (10%)
8. (15%) (a) Is the following circuit a Mealy or Moore state machine? (5%)  
(b) Construct a transition table or state graph for the following circuit. (10%)

