

國立臺北科技大學 113 學年度碩士班招生考試

系所組別：2110 電機工程系碩士班甲組

第一節 電路學 試題

第 1 頁 共 2 頁

注意事項：

1. 本試題共 10 題，其中 8 題每題 10 分，1 題 8 分，1 題 12 分，共 100 分。
2. 不必抄題，作答時請將試題題號及答案依照順序寫在答案卷上。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

1. In Figure 1, please find the maximum power transfer to R_L and what percentage of the total power generated by these two sources is delivered to R_L ? (10%)

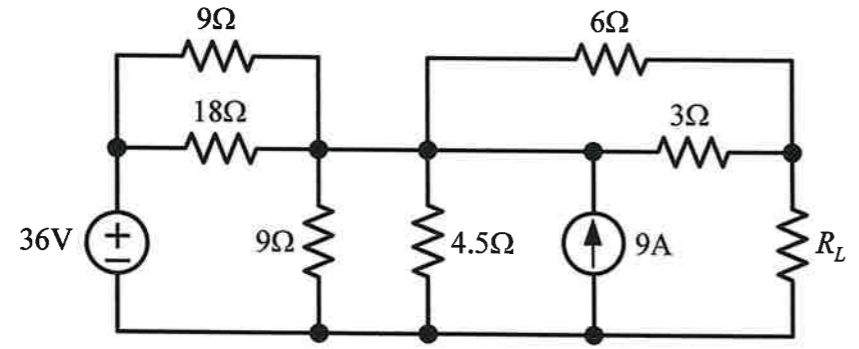


Figure 1.

2. In Figure 2, a 10V voltage source and a 5A current source are imposed on the circuit.
 (a) Please find the value of v_o based on the superposition principle.
 (b) If 10V is changed to 20V, and 5A is changed to 15A, then find the value of v_o . (5%, 5%)

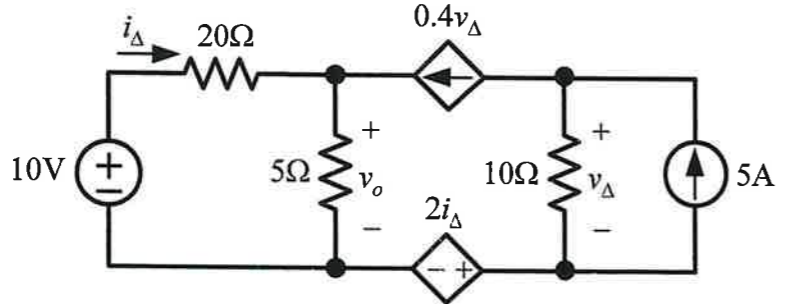


Figure 2.

3. In Figure 3, please find the current flowing through the 20H inductor, namely, $i_3(t)$. (10%)

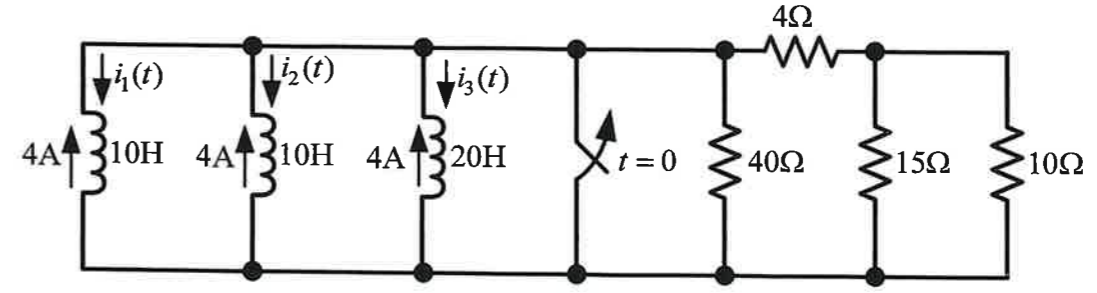


Figure 3.

4. In Figure 4, please find the value of $v_o(t)$ based on the phasor method. (10%)

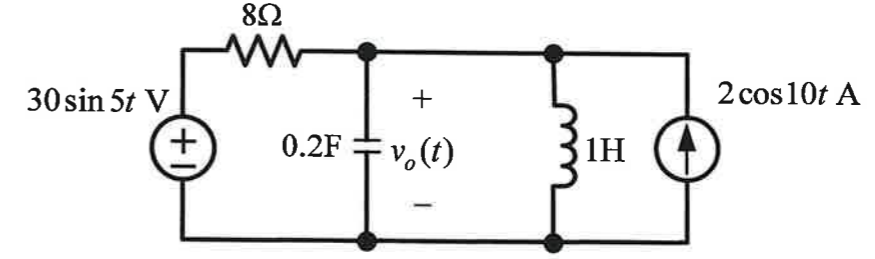


Figure 4.

5. If the impedance parameters, namely, z parameters, is expressed by $(Z) = \begin{pmatrix} 10\Omega & 7.5\Omega \\ 7.5\Omega & 9.375\Omega \end{pmatrix}$, then two identical circuits are connected in parallel as shown in Figure 5. Please find the value of I_L . (10%)

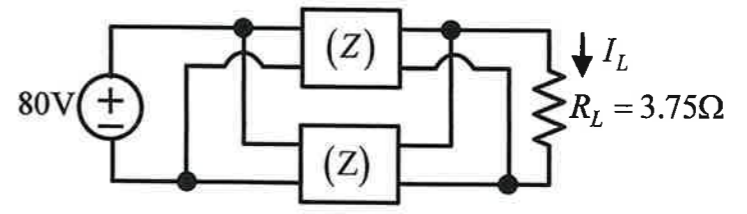


Figure 5.

6. In Figure 6, please find the expression of $v(t)$ with $I=0.1A$ for $t \geq 0$ (10%)

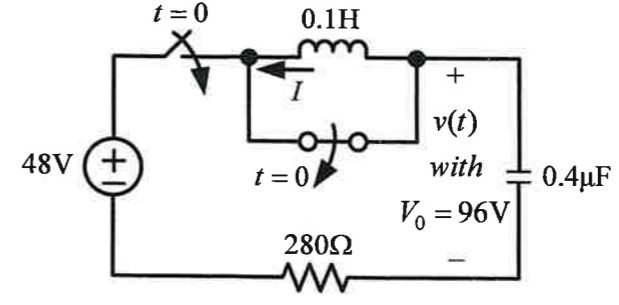


Figure 6.

注意：背面尚有試題

7. In Figure 7, (a) please find the (1) transient, (2) steady-state, (3) natural and (4) forced responses of $v(t)$, and (b) please find the (5) transient, (6) steady-state, (7) natural and (8) forced responses of $i(t)$. (1%*8)

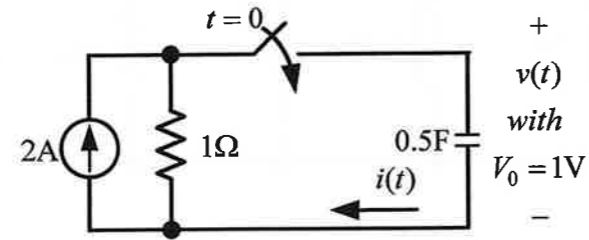


Figure 7.

8. In Figure 8, the ideal transformer is with the primary-side turns N_p versus the secondary-side turns N_s being $N_p : N_s = 5 : 4$. The voltages across the primary and secondary sides are expressed as v_p and v_s , respectively, and the current flowing through the primary and secondary sides are represented by i_p and i_s , respectively. Note that the answer must be expressed by the matrix form, namely, $\begin{pmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{pmatrix}$. If not, no score.

(a) Please find b parameters for a single transformer.

(b) Please find b parameters for two identical transformers connected in cascade. (5%, 5%)

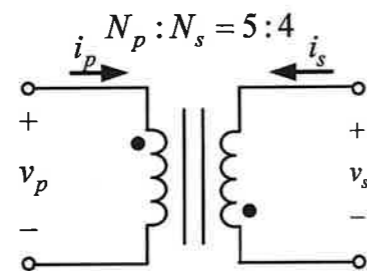


Figure 8.

9. In Figure 9, find the currents $i_1(t)$ and $i_2(t)$ at $t = \infty$, and the flux linkages $\lambda_1(t)$ and $\lambda_2(t)$ at $t = \infty$. (3%*4)

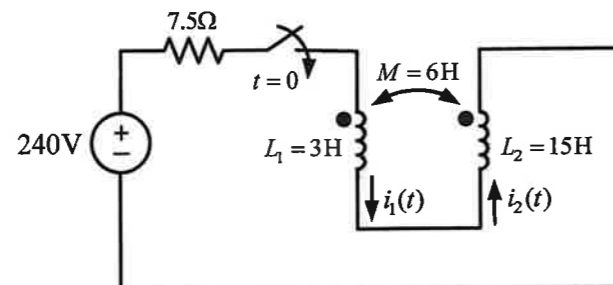


Figure 9.

10. Question and Answer (1%*10)

- (1) What main feature is required for a linear system?
- (2) What will happen if the KVL is not hold?
- (3) What will happen if the KCL is not hold?
- (4) Considering the linear circuit in the time domain, how is the output signal $y(t)$ expressed by the system signal $h(t)$ and the input signal $x(t)$?
- (5) Considering the linear circuit in the Laplace domain, how is the output signal $Y(s)$ expressed by the system signal $H(s)$ and the input signal $X(s)$?
- (6) What main constraint is required for the transfer function?
- (7) What main constraint is required for the Fourier series?
- (8) What three constraints are required when the phasor method is used?
- (9) Under the step response in the Laplace domain, what two time-domain responses can be obtained by the inverse Laplace transform of the corresponding output?
- (10) What is the physical meaning of the root-mean-square (RMS) value?