

國立臺北科技大學 113 學年度碩士班招生考試

系所組別：2151 電機工程系碩士班戊組


第一節 數位邏輯設計 試題 (選考)

第 1 頁 共 1 頁

注意事項：

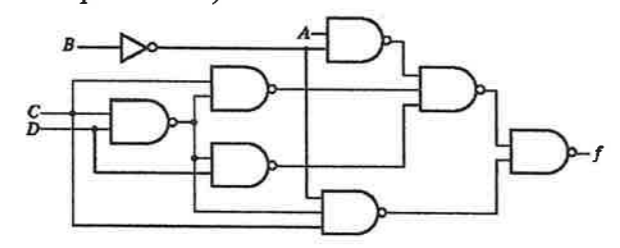1. 本試題共七題，共 100 分。
2. 不必抄題，作答時請將試題題號及答案依照順序寫在答案卷上。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

- 一、(15%) Assume $X_1 = -117$, $X_2 = D_{16}$, and $X_3 = 23_{10}$. The negative number is represented in 2's complement.
- (一) Convert X_1 , X_2 , and X_3 to 6-bit binary numbers with the most significant bit representing the sign. (5%)
 - (二) Work on the arithmetical operation: $X_1 + X_3 - X_2$ in binary. Indicate whether overflow occurs. (10%)
- 二、(20%) Simplify the following expressions to the minimal sum of products. Only individual variables should be complemented.
- (一) $b'c'd' + bcd + acd' + a'b'c + a'bc'd$ (5%)
 - (二) $F(V, W, X, Y, Z) = \Pi M(0, 3, 6, 9, 11, 19, 20, 24, 25, 26, 27, 28, 29, 30) \cdot \Pi D(1, 2, 12, 13)$ (5%)
 - (三) $(A + C' + F' + G)(A + C' + F + G)(A + B + C' + D' + G)(A + C + E + G)(A' + B + G)(B + C' + F + G)$ (10%)
- 三、(10%) Realizes f' of the following circuit containing only NOR gates (Only individual variables should be complemented)




- 四、(10%) Find a minimum two-level, multiple-output SOP circuits to realize the following functions. Use a PLA to implement the minimum SOP circuits. Specify the PLA table only.

$$f_1(a, b, c, d) = \Sigma m(3, 4, 6, 9, 11)$$

$$f_2(a, b, c, d) = \Sigma m(2, 4, 8, 10, 11, 12)$$

$$f_3(a, b, c, d) = \Sigma m(3, 6, 7, 10, 11)$$

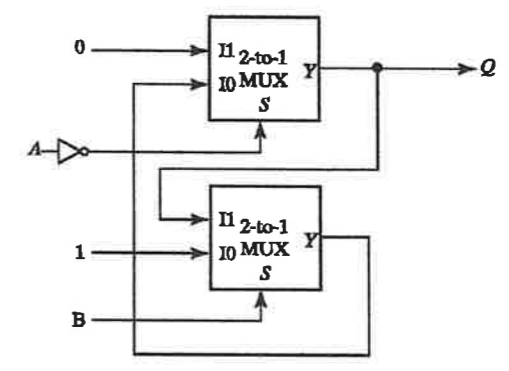- 五、(10%) (一) Construct a state table for the following circuit and identify the stable states of the circuit. (5%)
- (二) Derive a Boolean algebra equation for the next value of the output Q^+ in terms of Q , A and B . (5%)



- 六、(20%) An $M-N$ flip-flop works as follows:
- If $MN = 00$, the next state of the flip-flop is 0.
 - If $MN = 01$, the next state of the flip-flop is the same as the present state.
 - If $MN = 10$, the next state of the flip-flop is the complement of the present state.
 - If $MN = 11$, the next state of the flip-flop is 1.
- (一) Give the characteristic (next-state) equation for this flip-flop. (5%)
 - (二) Design a 3-bit counter by using $M-N$ flip-flops which counts in the sequence as follows. (10%)
 $CBA = 000, 001, 011, 111, 101, 100, (\text{repeat}) 000, \dots$
 - (三) What will happen if the counter of CBA is started in state 010? (5%)

- 七、(15%) (一) Is the following circuit a Mealy or Moore state machine? (5%)
- (二) Use T flip-flops to construct the following state machine. (10%)

