

# 國立臺北科技大學 100 學年度碩士班招生考試

系所組別：2401 光電工程系碩士班

第三節 電子學 試題 (選考)

第一頁 共二頁

### 注意事項：

1. 本試題共五題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

[1] 20%

A short-base diode is one where the widths of the p and n regions are much smaller than  $L_n$  and  $L_p$ , respectively. As a result, the excess minority-carrier distribution in each region is a straight line rather than the exponentials shown in Fig. 1.

(a) For the short-base diode, sketch a figure corresponding to Fig. 1, and assume, as in Fig. 1, that  $N_A \gg N_D$ . (5%)

(b) Show that if the widths of the p and n regions are denoted  $W_p$  and  $W_n$  then

$$I = Aqn_i^2 \left[ \frac{D_p}{(W_n - x_n)N_D} + \frac{D_n}{(W_p - x_p)N_A} \right] (e^{V/V_T} - 1)$$

and

$$Q_p = \frac{1}{2} \frac{(W_n - x_n)^2}{D_p} I_p \cong \frac{1}{2} \frac{W_n^2}{D_p} I_p, \text{ for } W_n \gg x_n. \text{ (5\%)}$$

(c) Also, assuming  $Q \cong Q_p$ ,  $I \cong I_p$ , show that

$$C_d = \frac{\tau_T}{V_T} I$$

where

$$\tau_T = \frac{1}{2} \frac{W_n^2}{D_p}. \text{ (5\%)}$$

(d) If a designer wishes to limit  $C_d$  to 8 pF at  $I = 1$  mA, what should  $W_n$  be? Assume  $D_p = 10 \text{ cm}^2/\text{s}$ . (5%)

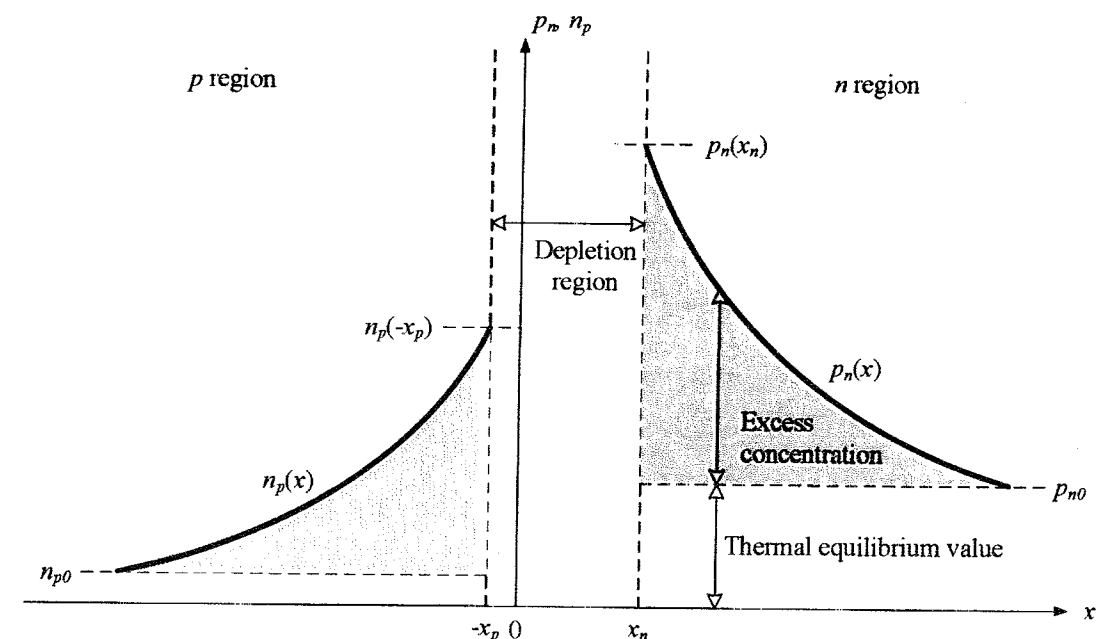


Fig. 1

[2] 20%

For the circuit of Figure 2, the OP-Amp has open-loop gain  $A_d = 10^4 \text{ V/V}$ , differential input resistance  $R_{id} = 100 \text{ K}\Omega$ , and incremental output resistance  $r_o = 1 \text{ K}\Omega$ . Please use the feedback method to find:

- (1) The voltage gain  $v_o/v_s$ . (5%)
- (2) The input resistance  $R_{in}$ . (5%)
- (3) The output resistance  $R_{out}$ . (5%)
- (4) What is the configuration of the feedback amplifier? (5%)

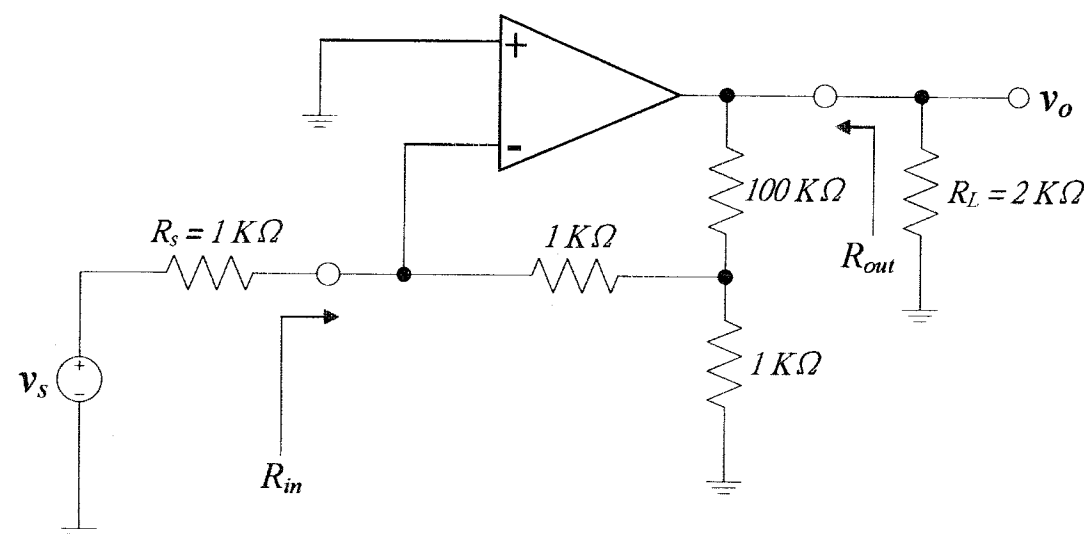


Fig. 2

注意：背面尚有試題

[3] 20%

For the circuit in Fig. 3,  $|V_T|=1V$ ,  $k'W/L=1mA/V^2$ ,  $h_{fe}=100$ , and the Early voltage magnitude for all devices (including those that implement the current sources) is  $100V$ . The signal source  $V_s$  has a zero dc component. Find the dc voltage at the output and at the base of  $Q_3$ . Find the values of  $A$ ,  $\beta$ ,  $A_f$ ,  $R_{in}$  and  $R_{out}$ .

 


Fig. 3

[4] 20%

For the circuit of Fig. 4. Please find:

- (1) The total gain  $A_{db, total}$  of this complete filter. (5%)
- (2) The bandwidth  $BW$  of this complete filter. (5%)
- (3) The center frequency  $f_0$  of this filter. (5%)
- (4) Draw the Bode plot for the complete filter. (5%)

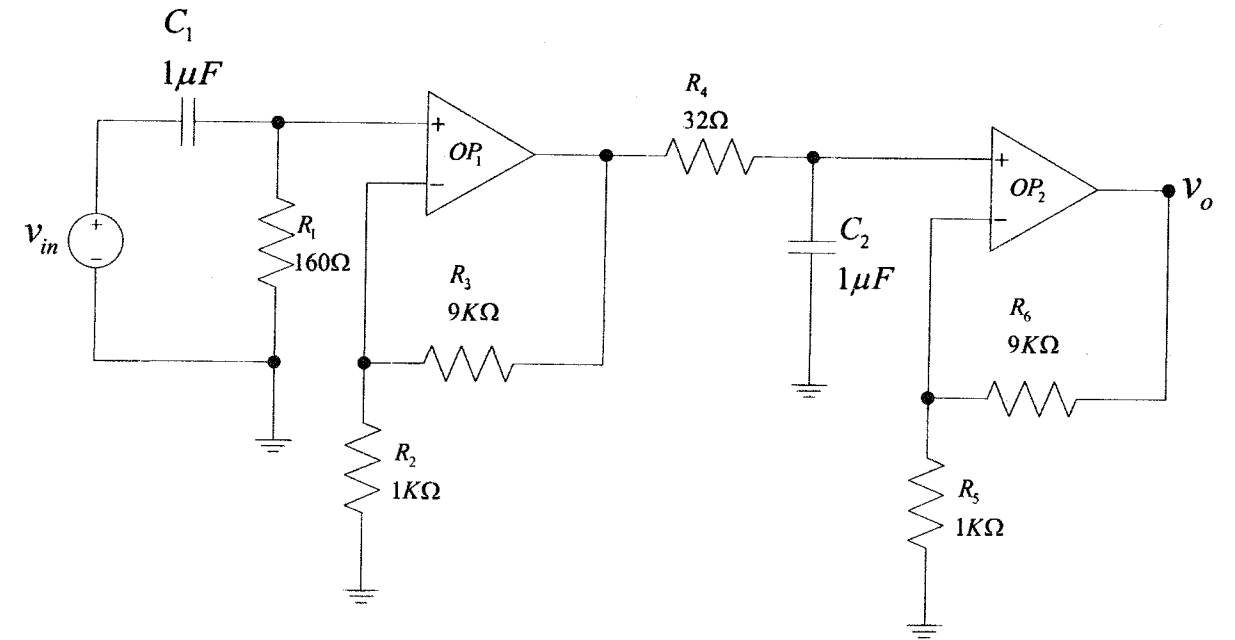


Fig. 4

[5] 20%

As shown in Figure 4, the schematic of a state-variable filter as shown contains passive elements and ideal operational amplifiers. Please derive the transfer functions of  $V_1(S)/V_i(S)$  (10%), and  $V_3(S)/V_i(S)$ . (10%)

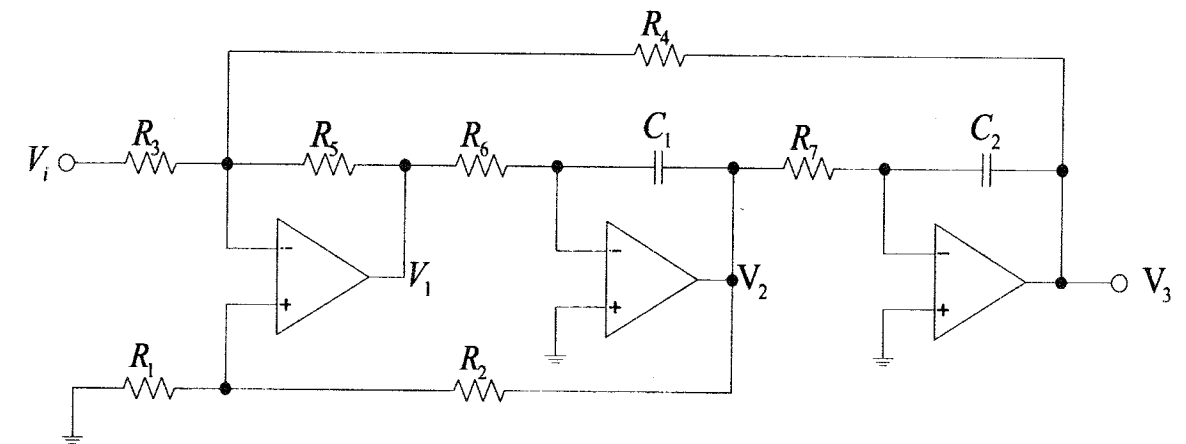


Fig. 5