

國立臺北科技大學
101 學年度研究所碩士在職專班招生

電腦與通訊研究所
丁組：電子學試題

填准考證號碼

--	--	--	--	--

第一頁 共二頁

注意事項：

1. 本試題共**【五】**題，配分共 100 分。
2. 請按順序標明題號作答，不必抄題。
3. 全部答案均須答在試卷答案欄內，否則不予計分。

1. For the circuit shown in figure 1, all of the operational amplifiers are ideal, please find the gain of the circuit, $\frac{v_o}{v_{i2} - v_{i1}} = ?$ (20%)

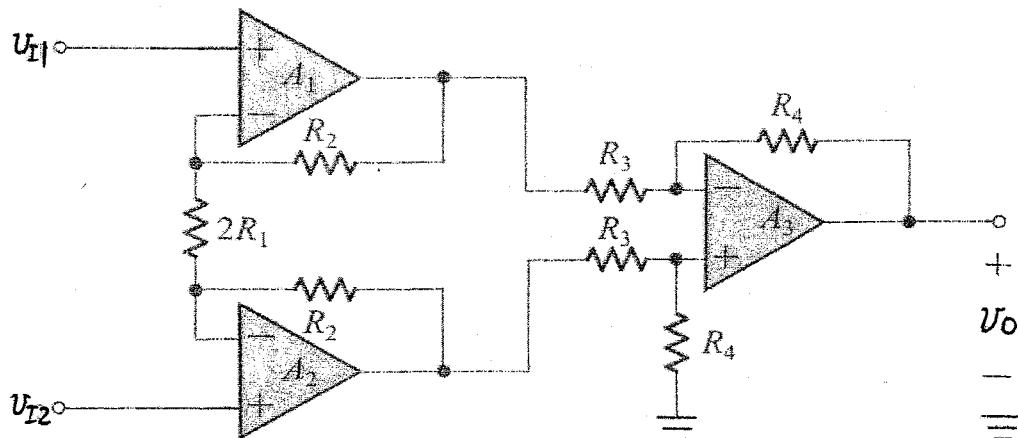


Figure 1

2. For the amplifier shown in figure 2, the MOSFET is without body effect. If the small-signal parameters of the MOSFET are $\frac{\partial I_D}{\partial V_{GS}} = g_m$, $\frac{\partial V_{DS}}{\partial I_D} = r_o = \infty$, and the capacitors C_{C1} and C_{C2} approach infinity, please find:

(1) voltage gain $\frac{V_o}{V_i} = ?$ (10%)

(2) input resistance $R_{in} = ?$ (5%)

(3) output resistance $R_{out} = ?$ (5%)

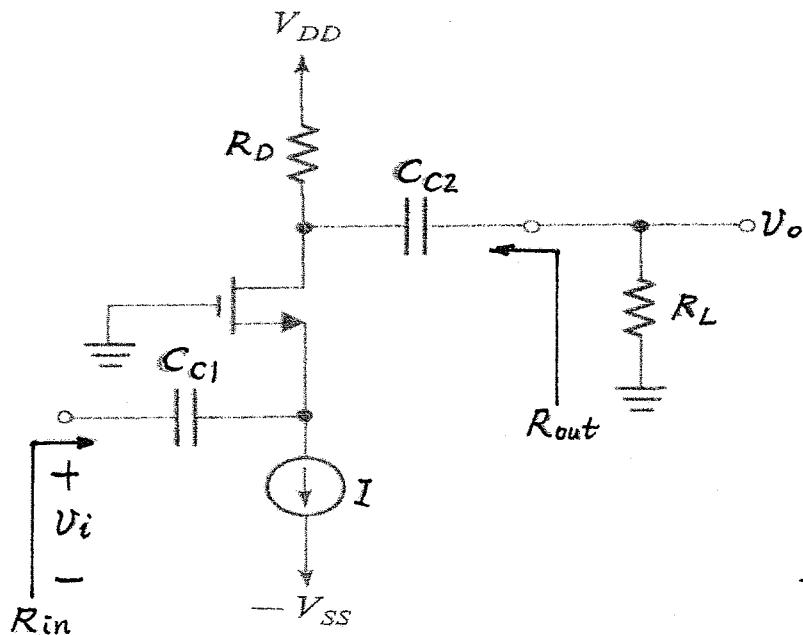


Figure 2

3. As shown in figure 3, the circuit is an oscillator. If all of the operational amplifiers are ideal, please derive the oscillation frequency $\omega_0 = ?$ (20%)

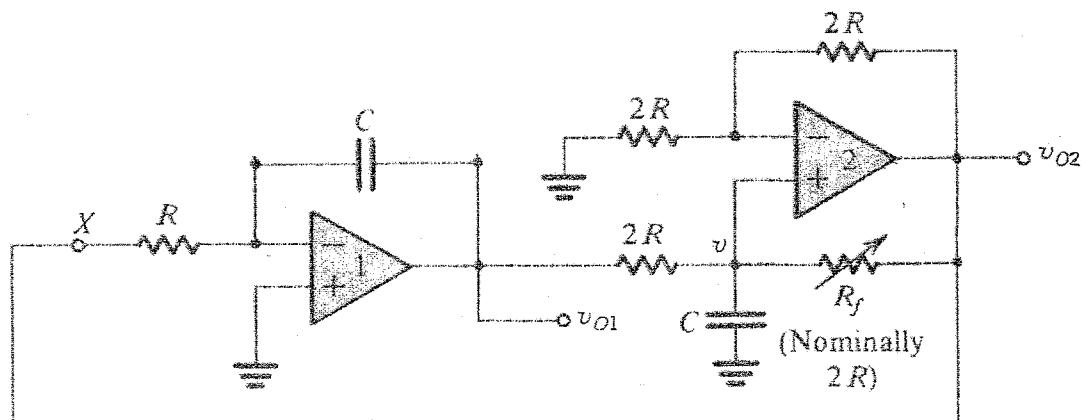


Figure 3

注意：背面尚有試題

4. For the circuit shown in figure 4, if the parameters of the transistor $\beta = 100$, $V_{BE} = 0.7V$, and its small-signal output resistance $r_o = \infty$, please find:

$$(1) \text{ voltage gain } \frac{V_o}{V_s} = ? \text{ (10\%)} \quad (1)$$

$$(2) \text{ input resistance } R_{in} = ? \text{ (5\%)} \quad (2)$$

$$(3) \text{ output resistance } R_{of} = ? \text{ (5\%)} \quad (3)$$

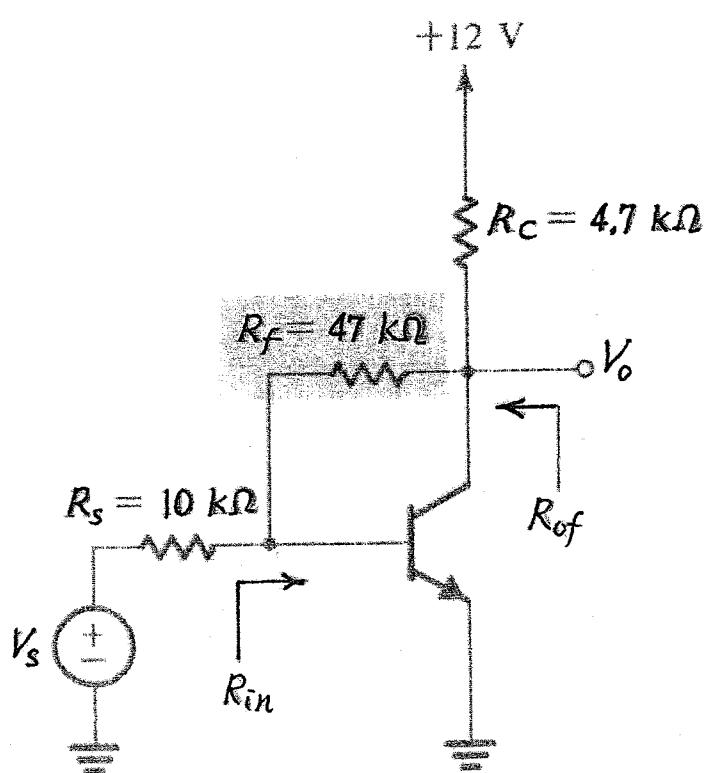


Figure 4

5. As shown in figure 5, the circuit is a CMOS inverter, the relationship of Q_N

and Q_P can be described as $\mu_n C_{ox} \left(\frac{W_N}{L_N} \right) = \mu_p C_{ox} \left(\frac{W_P}{L_P} \right)$, $V_m = |V_{tp}| = V_t$. Please find

the noise margins NM_H and NM_L (20%)

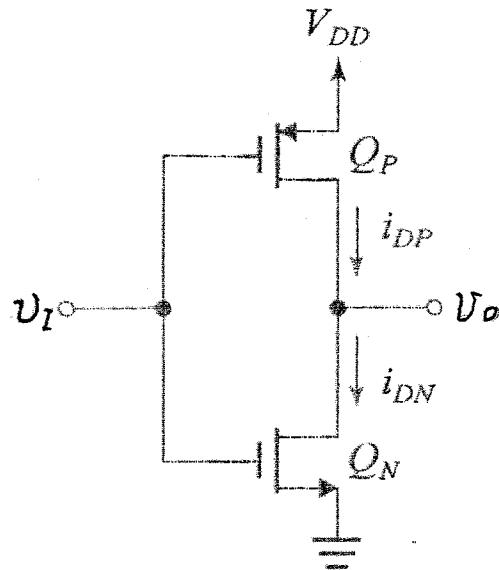


Figure 5