

國立臺北科技大學 102 學年度碩士班招生考試

系所組別：2230 電腦與通訊研究所丙組

第二節 電子學 試題

第一頁，共一頁

注意事項：

1. 本試題共五題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

1. Please calculate the input impedance (Z_{in}) of the diode-connected PMOS as shown in Fig. 1. Assume no body effect exists in the device. (10%)
2. Figure 2 shows a layout of a CMOS logic circuit.
 - (a) Sketch the schematic of Fig. 2, where a and b are the inputs, and out is the output (5%)
 - (b) What is the logic function in Fig. 2? (5%)
 - (c) Why NAND gate is preferably used in CMOS logic circuits as compared with NOR gate for the consideration of package density? (10%)
 - (d) Design the logic function $Y = \overline{AB} + A\overline{B}$ using NAND gates. (10%)
3. In the Fig. 3, the op-amp circuit has three internal critical frequencies as follow: 1.2KHz, 50KHz, and 250KHz. If the midrange open-loop gain is 100dB, is the amplifier configuration stable, marginally stable, or unstable? (15%)

 


Fig. 1

 


Fig. 2

 


Fig. 3

4. For the circuit shown in Fig.4, let $V_{BE(on)}=0.7V$, $\beta=100$, and $V_{CE(sat)}=0.2V$.

- (a) Determine the Q -point of the circuit. (10%)
- (b) Plot the load line and indicate the Q -point on the collector current-voltage characteristic plot. Indicate important data and the associated units on the plot. (10%)

5. Fig. 5 shows a feedback circuit. Please find:

- (a) The feedback topology? (5%)
- (b) $|\beta A|$ (5%)
- (c) V_o/V_s (5%)
- (d) R_{out} (5%)
- (e) R_{in} (5%)

 


Fig. 4

 


Fig. 5