

國立臺北科技大學  
100 學年度研究所碩士在職專班入學考試

電腦與通訊研究所  
丁組：電子學試題

填准考證號碼

--	--	--	--	--	--	--	--

第一頁 共一頁

**注意事項：**

1. 本試題共四題，配分共 100 分。
2. 請按順序標明題號作答，不必抄題。
3. 全部答案均須答在試卷答案欄內，否則不予計分。

一、 Consider the design of a CMOS exclusive or gate.

1. Write the logic function of an exclusive or gate with input A and B. (5%)
2. Design and sketch the exclusive or gate by means of NAND gates. (5%)
3. Simplify the below logic function. (5%)

$$Y = BC + AB(\bar{C} + D) + AD(\bar{B} + BC) + BC(A + \bar{D}) + B(\bar{A}C + \bar{A}CD)$$

4. Design and sketch the above logic function by means of NAND gates. (5%)

二、 Please design the requested circuit and sketch the schematic:

1. Use NAND gates, resistors and capacitors to design a power-on-reset circuit. (10%)
2. Use op-amps and resistors to design an instrumentation amplifier with 40dB voltage gain. (10%)
3. Use capacitors and diodes to design a voltage doubler. (10%)

三、 Fig.1 shows an output stage of a CMOS op-amp, where  $V_{DD} = 5V$ ,  $V_{Bias} = 2.5V$  and  $C_L = 1nF$ . Please use these parameters of MOS  $|V_{TN}| = |V_{TP}| = 0.7V$ ,

$\beta_n = \beta_p = 100 \mu A/V^2$  and  $V_A = 100V$  of MOS to calculate the following questions.

$$\beta = \mu C_{ox} \frac{W}{L}$$

1. Calculate the input "trip point", which means that the input voltage starts to make  $V_{out}$  change sharply. (10%)
2. Calculate the small signal gain  $A_v = v_o/v_{in}$  when operating at the trip point. (10%)
3. Calculate the negative slew rate when  $v_o$  decreases from high to low. (5%)

 


Fig.1

四、 According to the active filter shown in Fig.2, please answer the following questions:

1. Find the DC gain of  $V_o/V_{in}$ . (5%)
2. Find the transfer function of the voltage gain. (5%)
3. Find the input impedance. (5%)
4. Sketch its magnitude frequency-response characteristics. (5%)
5. Sketch its phase frequency-response characteristics. (5%)

 


Fig.2