

# 國立臺北科技大學 101 學年度碩士班招生考試

系所組別：1111、1132 機電整合研究所甲、丙組

## 第二節 電子學 試題 (選考)

第一頁 共三頁

### 注意事項：

1. 本試題共 9 題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

1. Describe the output wave form for the diode limiter as the following **Figure (1)**. (9%)

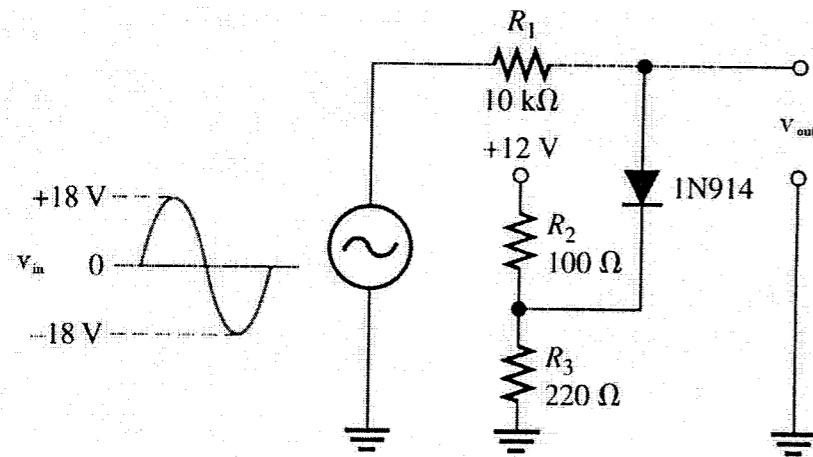


Fig. 1

2. Please answer the following questions as shown in the **Figure (2)**. (15%)

- (a) What is  $V_{CE} = ?$  when  $V_{in} = 0$  V
- (b) What minimum value of  $I_B$  is required to saturate this transistor if  $\beta_{DC}$  is 200 Neglect  $V_{CE(sat)}$
- (c) Calculate the maximum value of  $R_B$  when  $V_{IN} = 5$  V.

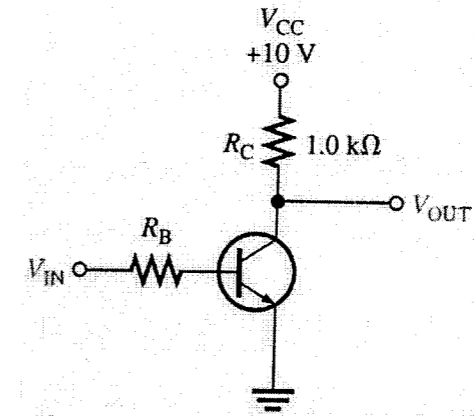


Fig. 2

3. The LED in the **Figure 3** requires 30mA, determine the amplitude of the square wave input voltage necessary to make sure that the transistor saturates. (if  $V_{CE(sat)} = 0.3$  V,  $\beta_{DC} = 50$ ,  $V_{LED} = 1.6$  V) (10%)

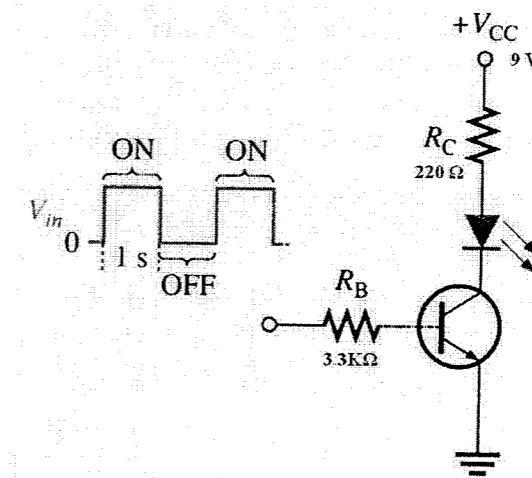


Fig. 3

4. Determine  $V_{EC}$  and  $I_C$  for the PNP transistor circuit in the **Figure 4** (10%)

注意：背面尚有試題

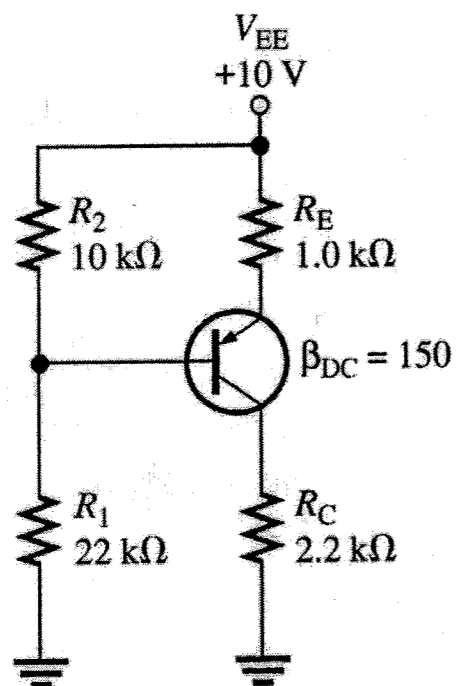


Fig. 4

5. Considering Op-AMPs with negative feedback, Please answer the following questions (Aol: Gain of open-loop OP, Aol is typically large,) (10%)
- As shown in figure 5 (a), determine the  $V_o = ?$
  - As shown in figure 5(b), determine the  $V_o = ?$

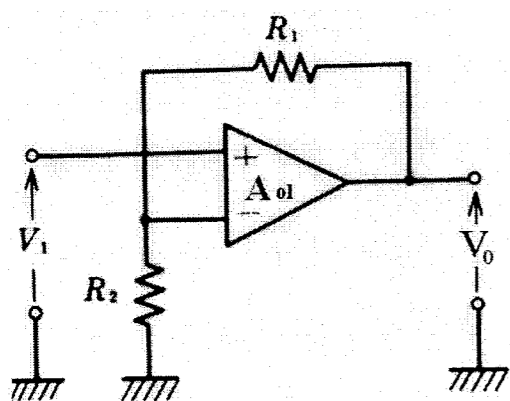


Fig. 5 (a)

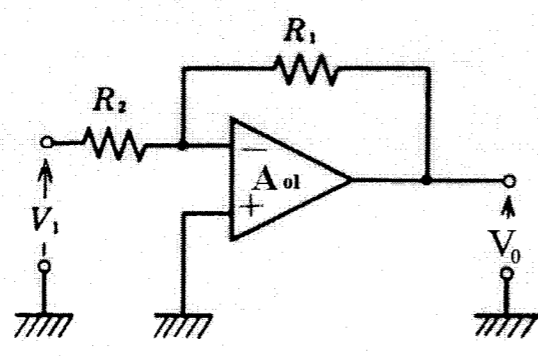


Fig. 5 (b)

6. Derive the  $V_o$  as a function  $V_1$  and  $V_2$  in the following **Figure 6**. (Assume that the gain Aol of OP open-loop is typically large) (10%)

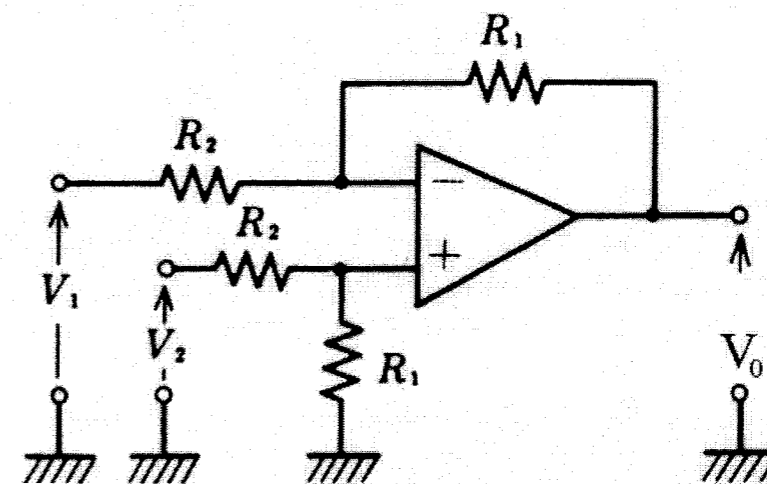


Fig. 6

7. The input signal in Fig. 7 (a) is applied to the comparator in the figure 7(b), Please drawing the output showing its proper relationship to the input signal. Assume the maximum output levels of the comparator are  $\pm 14V$  (10%)

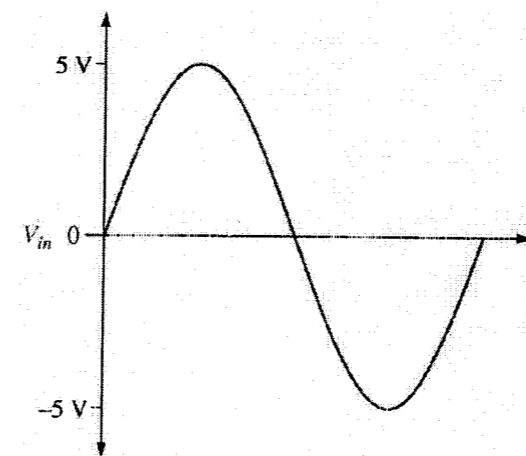


Fig. 7 (a)

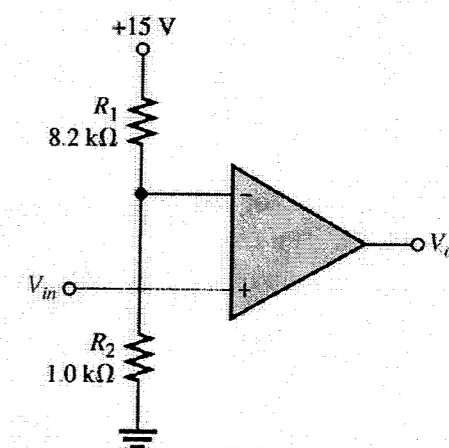


Fig. 7 (b)

8. For the circuit in **Figure 8** (16%)
- Find the mathematical expression for the transient behavior of the voltage  $V_c$  and the current  $i_c$  if the capacitor initially uncharged and switch is thrown into position 1 at  $t=0$  ms
  - Find the mathematical expression for the transient behavior of the voltage  $V_c$  and the current  $i_c$  if the capacitor initially uncharged and switch is thrown into position 2 at  $t=10$  ms (Assume that there is no leakage current of capacitor)
  - Find the mathematical expression for the transient behavior of the voltage  $V_c$  and the current  $i_c$  if the capacitor initially uncharged and switch is thrown into position 3 at  $t=20$  ms
  - Plot the waveforms obtained in the part (a)~(c) on the same time axis using the defined polarities in figure 8.

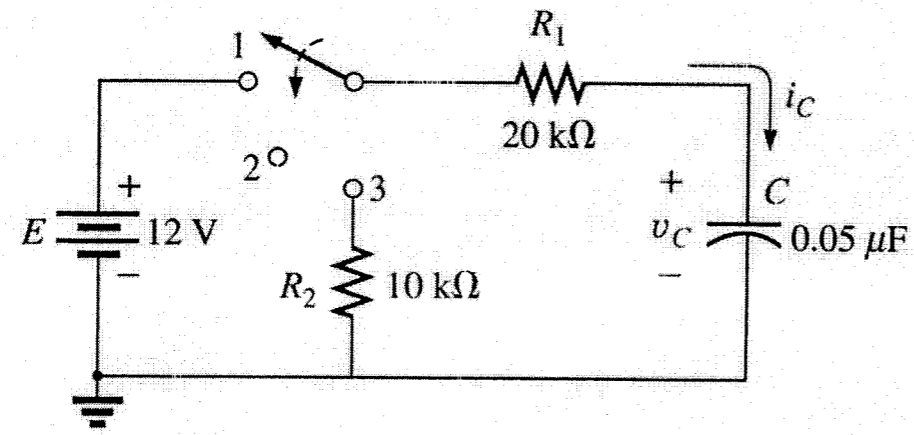


Fig. 8

9. Determine the following for the fixed-bias configuration of **Figure 9**. (10%)

- (a)  $I_B$  and  $I_C$
- (b)  $V_{CE}$
- (c)  $V_B$  and  $V_C$

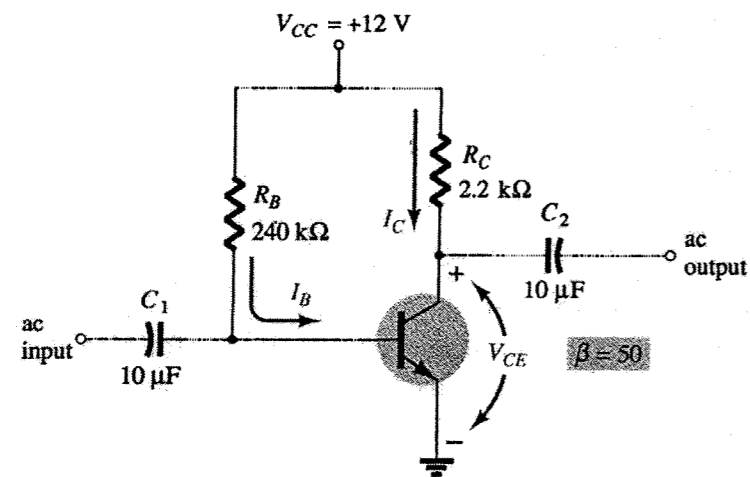


Fig. 9

