

國立臺北科技大學 101 學年度碩士班招生考試

系所組別：1523 自動化科技研究所乙組


第二節 電路學 試題 (選考)

第一頁 共一頁


注意事項：

1. 本試題共六題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

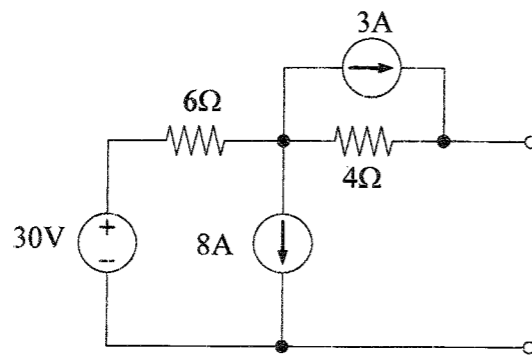1. For the circuit shown below, find the Thévenin equivalent circuit. (20%)




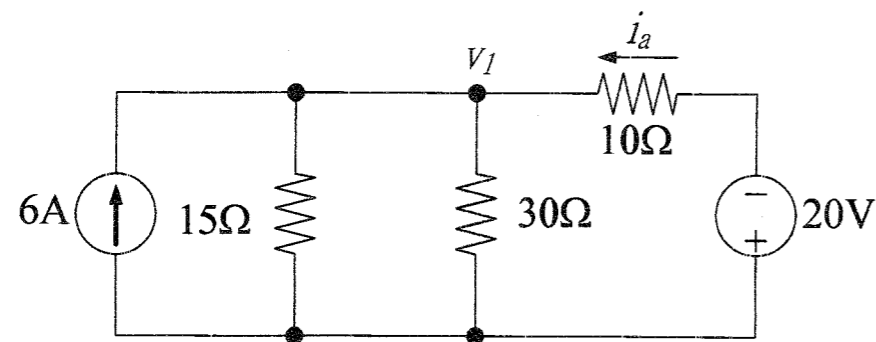2. Find the values of v_1 and i_a in the circuit shown below. (20%)




3. Evaluate the impedance and admittance of a 25 mH inductor when $\omega=800$ rad/s. Also find the voltage, $v(t)$, at the two terminals of the inductor when the current through the inductor is given as $i(t)=4 \cos(800t - 50^\circ)$. (20%)

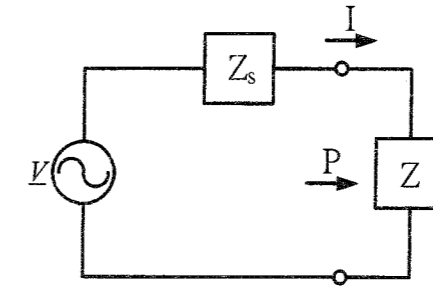4. For the circuit shown below, the impedance of the AC voltage source is $Z_s=R_s+jX_s$. The impedance of the load is $Z=R+jX$. The frequency of the AC source is ω rad/s. Express the real power P in terms of the fixed RMS source voltage, V , and impedances of the voltage source and the load. (10%)



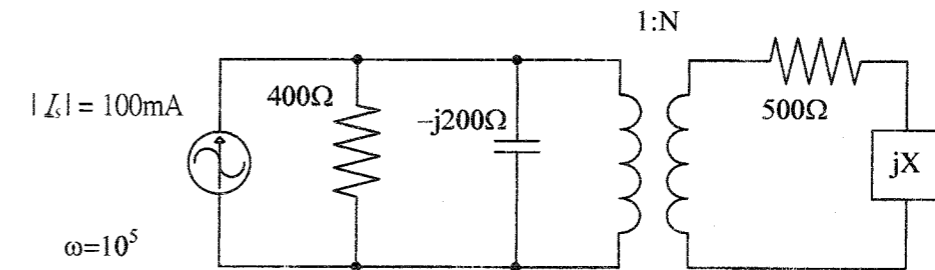5. The circuit shown below is the frequency domain model for the output of an amplifier operating at $\omega=10^5$. The load has a fixed resistance of 500Ω . Identify the load reactance X and the transformer's turn ratio N to achieve the maximum power transfer. Assume that the transformer is an ideal transformer. (20%)



6. For the circuit shown below, calculate the power factor. (10%)

