

國立臺北科技大學 101 學年度碩士班招生考試

系所組別：2120 電機工程系碩士班乙組

第一節 電路學 試題

第一頁 共二頁

注意事項：

1. 本試題共五題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

1. Please find the complete responses $v(t)$ and $i(t)$ and for $t > 0$ for the circuit as below in which $u(t)$ is the unit step function. Assume the circuit is at steady state at $t = 0^-$. 20%

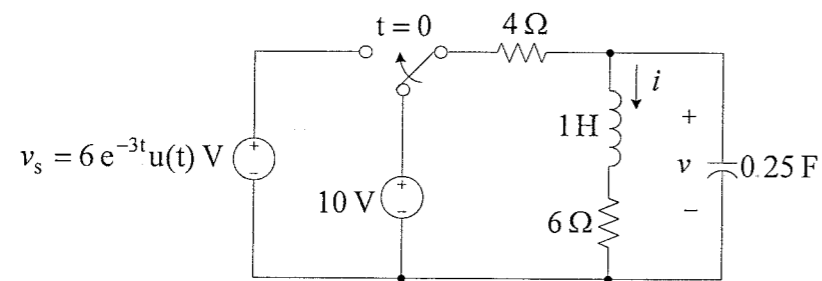


Fig.1

2. Suppose that the circuit shown in Fig. 2 was built using $R = 2 \text{ k}\Omega$ and that the voltage labeled v was measured to be $v = -1.87 \text{ V}$. Next, the resistor labeled R was changed to $R = 5 \text{ k}\Omega$, and the voltage v was measured to be $v = -3.0 \text{ V}$. Finally, the resistor was changed to $R = 10 \text{ k}\Omega$, and the voltage was measured to be $v = -3.75 \text{ V}$. How can these measurements be checked to verify that they are consistent? 20%

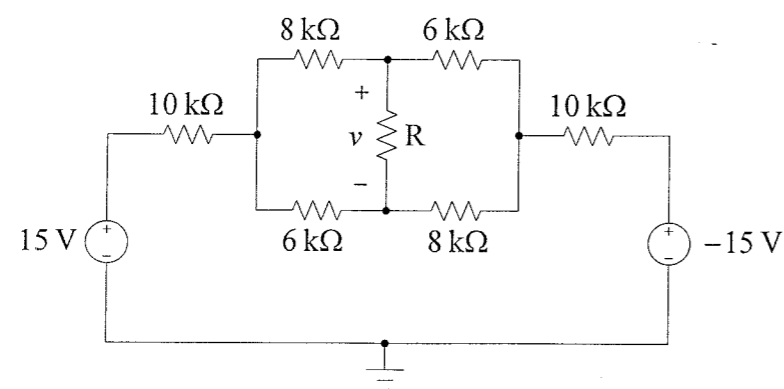


Fig. 2

3. A strain gauge bridge in Fig. 3 has a nominal resistance of $R = 120 \Omega$ which is the resistance when the strain is zero. This resistance is expected to increase or decrease by no more than 2Ω due to strain and the output voltage v_o is required to vary from -10 V to $+10 \text{ V}$ as ΔR varies from -2Ω to $+2 \Omega$. If the voltmeter is modeled as an ideal one. Please determine the amplifier gain k , needed to cause v_o to be related to ΔR by

$$v_o = 5 \Delta R$$

and please verify the proposed solution. 20%

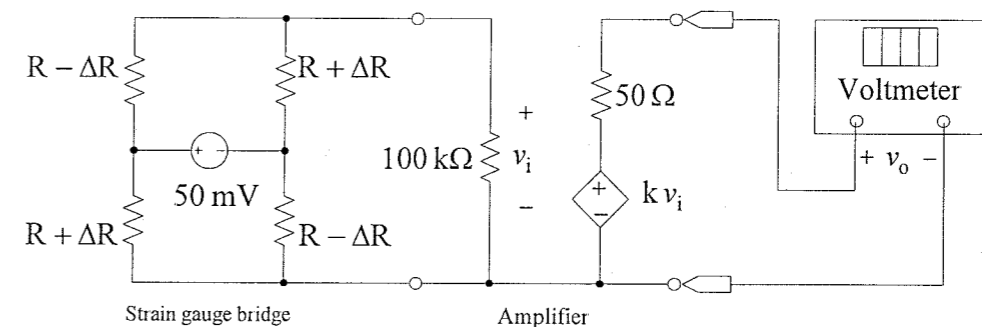


Fig. 3

4. Please find the forced response v in Fig. 4 if

$$v_g = 100 \cos(2000t) \text{ V}$$

20%

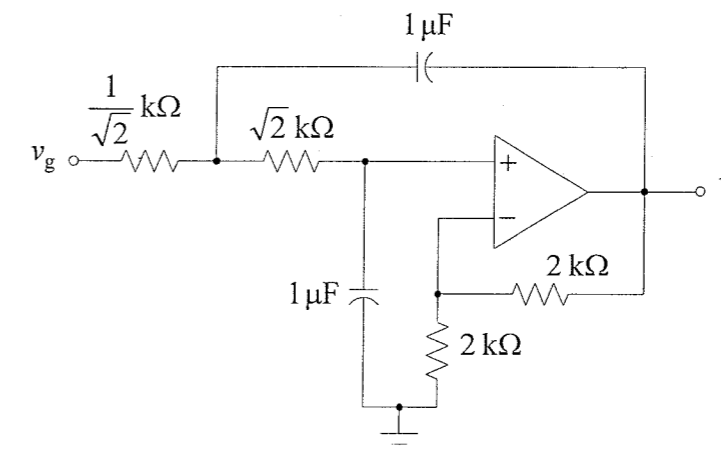


Fig. 4

注意：背面尚有試題

5. Please find the z-parameters for the phasor circuit of Fig. 5. 20%

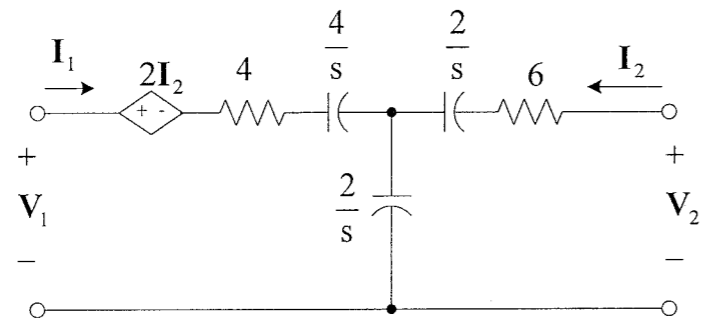


Fig. 5