

# 國立臺北科技大學 101 學年度碩士班招生考試

系所組別：2401 光電工程系碩士班

第三節 電子學 試題 (選考)

第一頁 共二頁

### 注意事項：

1. 本試題共七題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

1. (10%) Answer the following questions.
  - (1) What is the difference between drift current and diffusion current? (2%)
  - (2) Please draw the distribution of space charge and electric field in the depletion region of the pn junction. (4%)
  - (3) Please indicate the difference between NMOS and PMOS. (2%)
  - (4) Please give the definition of common-mode rejection ratio (CMRR). (2%)
2. (15%) Consider the circuit shown in Fig. P2.
  - (1) Please derive the overall transfer function  $T(s)=V_o(s)/V_s(s)$ . (6%)
  - (2) Provide the Bode magnitude plot for  $|T(j\omega)|$ . (6%)
  - (3) What is the bandwidth between 3-dB cutoff points? (3%)
3. (15%) Fig. P3 shows the common-gate amplifier.
  - (1) Find the input resistance  $R_{in}$ , the output resistance  $R_{out}$ , and the voltage gain  $A_v$ . (12%)
  - (2) Find the 3-dB frequency using open-circuit time-constant method. (3%)

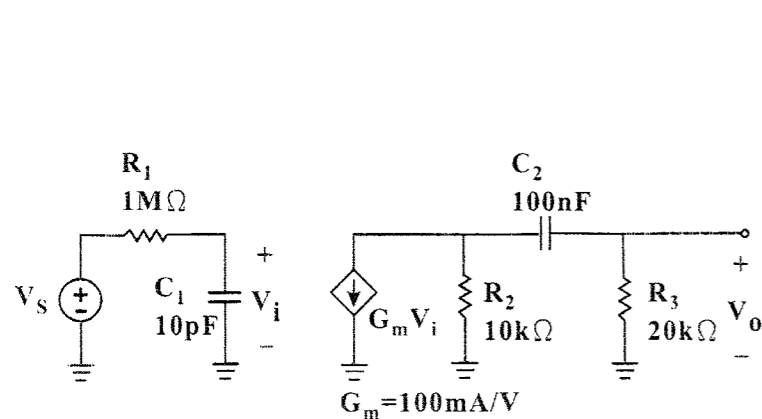


Fig. P2

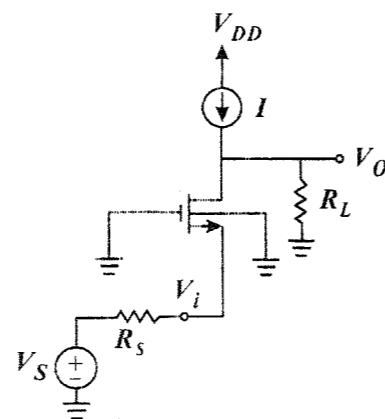


Fig. P3

4. (15%) Fig. P4 shows the logic inverter based on the differential pair. All transistors have  $V_{BE}=0.7V$  at  $I_C=1mA$  and have  $\beta=100$ .
  - (1) For  $v_i$  sufficiently low such that  $Q_1$  is cut off, find the value of the output voltage  $v_o$  ( $V_{OH}$ ). (3%)
  - (2) For  $v_i$  sufficiently high such that  $Q_1$  is carrying all the current  $I$ , find the value of the output voltage  $v_o$  ( $V_{OL}$ ). (3%)
  - (3) Determine the value of  $v_i$  that results in  $Q_1$  conducting 1% of  $I$  ( $V_{IL}$ ). (3%)
  - (4) Determine the value of  $v_i$  that results in  $Q_1$  conducting 99% of  $I$  ( $V_{IH}$ ). (3%)
  - (5) Calculate the values of the noise margins  $NM_H$  and  $NM_L$ . (3%)
5. (15%) Fig. P5 shows the CC-CB amplifier. The effects of  $r_x$  and  $r_o$  are neglected.
  - (1) Plot the simplified high-frequency equivalent circuit. (5%)
  - (2) Find the input resistance  $R_{in}$  and the overall voltage gain  $V_o/V_s$ . (5%)
  - (3) Derive the two poles for the CC-CB amplifier and its 3-dB frequency. (5%)

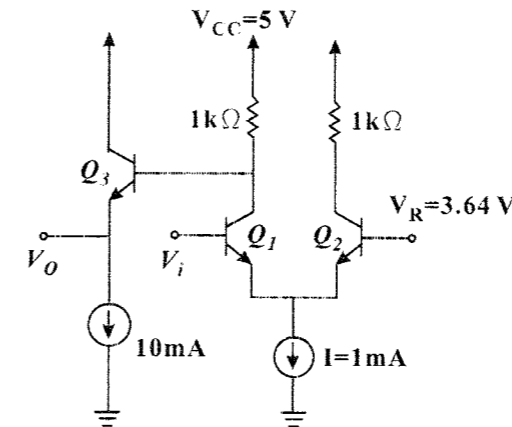


Fig. P4

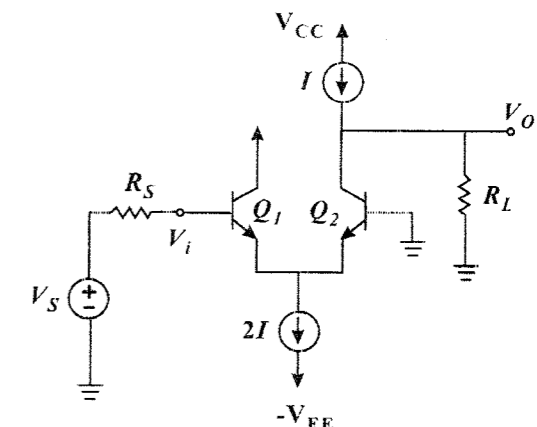


Fig. P5

6. (15%) Fig. P6 shows a feedback amplifier without details of the bias circuit.
  - (1) Sketch the A circuit and the circuit for determining  $\beta$ . (4%)
  - (2) Find the voltage gain, the input resistance, and the output resistance of A circuit. (8%)
  - (3) When  $A\beta$  is large, show the closed-loop voltage gain is  $A_f \equiv V_o/V_s \cong (R_F + R_E)/R_E$ . (3%)

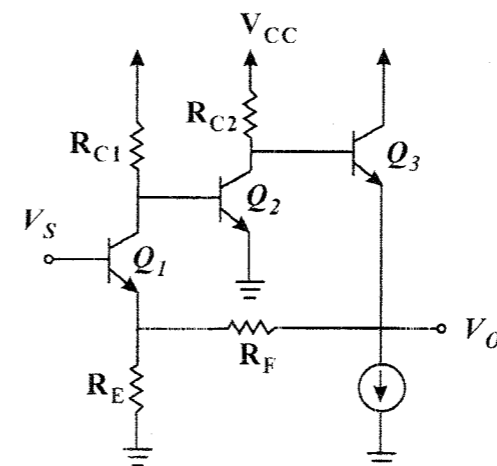


Fig. P6

注意：背面尚有試題

7. (15%) Consider the circuit in Fig. P7, find  $L(s)$ ,  $L(j\omega)$ , the frequency for zero loop phase, and  $R_2/R_1$  for oscillation.

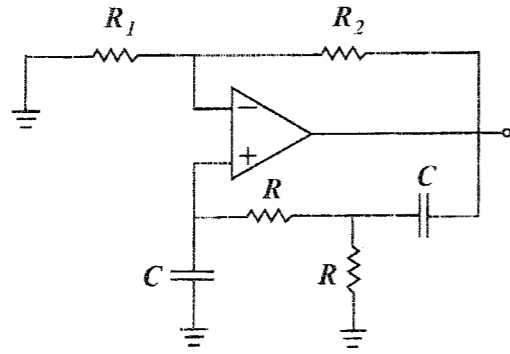


Fig. P7