

國立臺北科技大學 103 學年度碩士班招生考試

系所組別：2240 電子工程系碩士班丁組

第二節 數位邏輯設計 試題

第一頁 共一頁

注意事項：

1. 本試題共五題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

- 一、Convert the following decimal numbers to their hexadecimal equivalents.
 1. $(709)_{10}$ (5%)
 2. $(1889)_{10}$ (5%)
 3. $(4095)_{10}$ (5%)
 4. $(4096)_{10}$ (5%)
- 二、Suppose you wish to design a circuit that indicates when at least three out of four inputs are HIGH. The circuit has four inputs, D_3, D_2, D_1, D_0 and an active-HIGH output, Y. Write the Boolean expression for the circuit and draw the logic circuit. (20%)
- 三、Write the Boolean expression describing an 8 to 1 multiplexer. Evaluate the equation for the case where input D_5 is selected. (20%)
- 四、Draw a timing diagram for a NOR latch showing each of the following sequences of events:
 1. S and R are both HIGH, S goes LOW before R. (5%)
 2. S and R are both HIGH, R goes LOW before S. (5%)
 3. S and R are both HIGH, S and R go LOW simultaneously. (5%)
 4. State why $S=R=1$ is a forbidden state for the NOR latch. (5%)
- 五、Design a synchronous mod-10 counter, using positive edge-triggered D flip-flops. Check that unused states properly enter the main sequence. Draw a state diagram showing the unused states. (20%)