

國立臺北科技大學 103 學年度碩士班招生考試

系所組別：2401 光電工程系碩士班

第三節 電子學 試題 (選考)

第一頁 共二頁

注意事項：

1. 本試題共六題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

1. [15%]

For the circuit in *Figure 1*, we wish to select appropriate values for C_{C1} , C_{C2} , and C_E , which has $R_B = 100 \text{ k}\Omega$, $R_C = 8 \text{ k}\Omega$, $R_L = 5 \text{ k}\Omega$, $R_{sig} = 5 \text{ k}\Omega$, $\beta = 100$, $g_m = 40 \text{ mA/V}$, and $r_\pi = 2.5 \text{ k}\Omega$. It is required to have $f_L = 100 \text{ Hz}$.

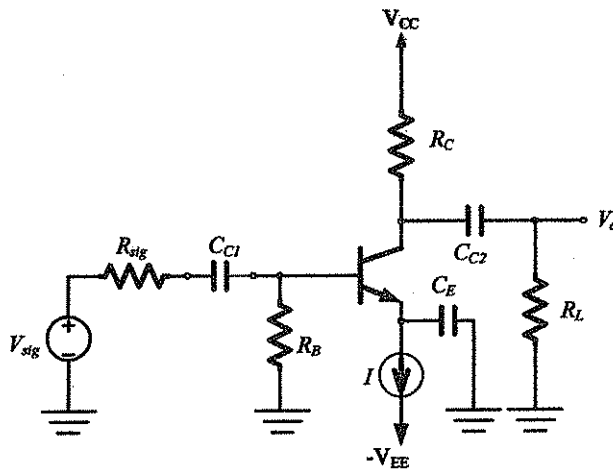


Figure 1

2. [10%]

For the circuit in *Figure 2*, let diode cut-in voltages are $V_r = 0.6 \text{ V}$ and assume the input voltage varies over the range $0 \leq v_i \leq +10 \text{ V}$. Plot V_O versus V_i .

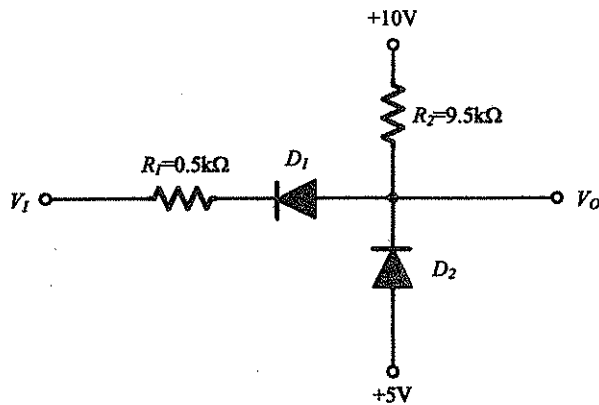


Figure 2

3.[10%]

Calculate the built-in potential and the depletion width for a silicon p-n junction diode with N_A (acceptor) = 10^{18} cm^{-3} and N_D (donor) = 10^{15} cm^{-3} at 300 K. Given silicon dielectric constant $\epsilon_{\text{si}} = 11.7 \times 8.85 \times 10^{-14} \text{ F/cm}$, $q = 1.6 \times 10^{-19} \text{ coul}$, $n_i^2 = 1 \times 10^{20} \text{ cm}^{-6}$, $kT/q = 25 \text{ mV}$.

4.[20%]

Transistor Q_1 in the circuit of *Figure 4* is operating as a CE amplifier with an active load provided by transistor Q_2 , which is the output transistor in a current mirror formed by Q_2 and Q_3 .

(a) Neglecting the finite base currents of Q_2 and Q_3 and assuming that their $V_{BE} \cong 0.7 \text{ V}$ and that Q_2 has five times the area of Q_3 , find the value of I .

(b) If Q_1 and Q_2 are specified to have $|V_A| = 50 \text{ V}$, find r_{o1} and r_{o2} and hence the total resistance at the collector of Q_1 .

(c) Find $r_{\pi 1}$ and g_{m1} assuming that $\beta_1 = 50$.

(d) Find R_{in} , A_v , and R_o .

注意：背面尚有試題

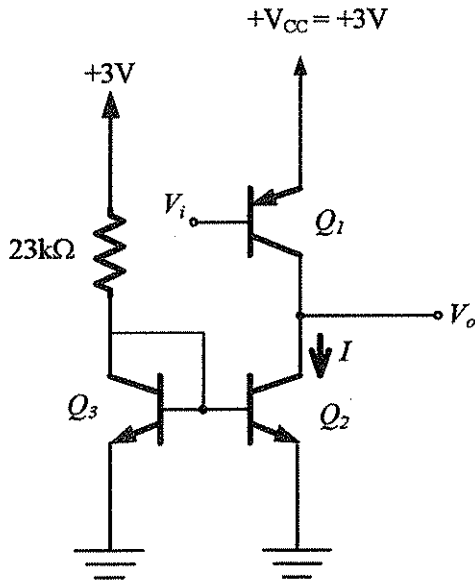


Figure 4

5.[25%]

Figure 5 shows a feedback current amplifier formed by cascading an inverting voltage amplifier μ with a MOSFET Q . The output current I_o is the drain current of Q . The feedback network, consisting of resistors R_1 and R_2 , senses an exactly equal current, namely, the source current of Q , and provides a feedback current signal that is mixed with I_s at the input node. Note that the bias arrangement is not shown.

The amplifier μ can be implemented in a variety of ways, including by means of an op amp, a differential amplifier, or a single-ended inverting amplifier. The simplest approach is to implement μ with a CS MOSFET amplifier. However, in such a case the loop gain will be very limited. Assume that the amplifier μ has an input resistance R_{id} , an open-circuit voltage gain μ , and an output resistance r_{o1} .

If the loop gain is large, find numerical values for A_f , R_i , R_{in} , R_o , and R_{out} for the following case: $\mu = 1000$ V/V, $R_s = \infty$, $R_{id} = \infty$, $r_{o1} = 1$ k Ω , $R_1 = 10$ k Ω , $R_2 = 90$ k Ω , and for Q : $g_m = 5$ mA/V and $r_o = 20$ k Ω . (5% each)

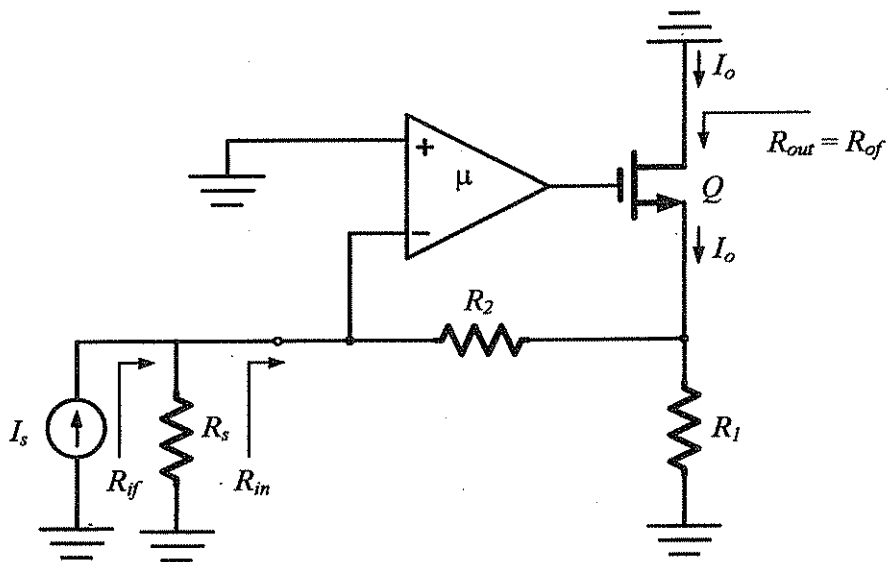


Figure 5

6.[20%]

The active biquard filter as shown contains passive elements and ideal operational amplifiers, as shown in *Figure 6*. Please derive the transfer functions of $V_o(s)/V_i(s)$.

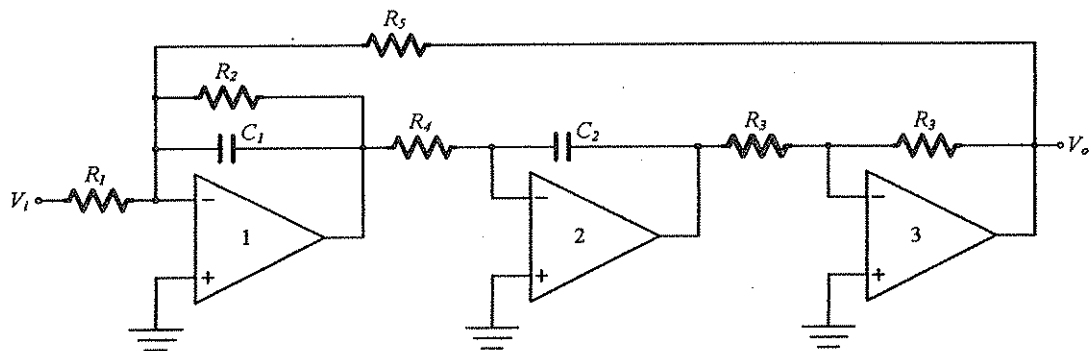


Figure 6