

# 國立臺北科技大學

## 九十二學年度光電技術研究所入學考試

### 電子學試題

填准考證號碼

第一頁 共二頁

--	--	--	--	--	--	--	--	--	--

#### 注意事項：

1. 本試題共【8】題，配分共100分。
2. 請按順序標明題號作答，不必抄題。
3. 全部答案均須答在答案卷之答案欄內，否則不予計分。

1. [10%]

Figure 1 shows a generalization of the noninverting configuration, where a resistive network having a transfer function  $\beta \equiv V_1/V_0$  is connected in the negative feedback path of the op amp.

- (a) Show that if the open-loop gain  $A$  is infinite, then the closed-loop gain  $V_0/V_s = 1/\beta$ . (3%)
- (b) Derive an expression for the closed-loop gain assuming  $A$  is finite. (3%)
- (c) If the op amp is internally compensated such that  $A \approx \omega_t/s$ , show the 3-dB frequency  $f_{3dB}$  of the closed-loop gain is  $\beta f_t$ . (4%)

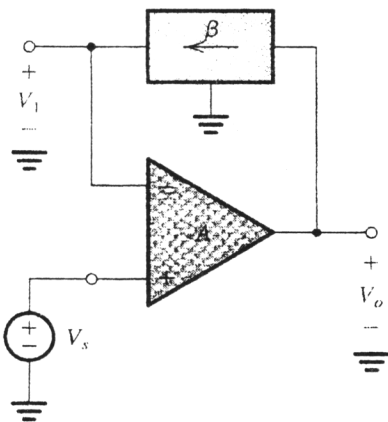


Fig. 1

2. [10%]

Assuming the diodes to be ideal, find the values of  $I$  and  $V$  in the circuits of Fig. 2.

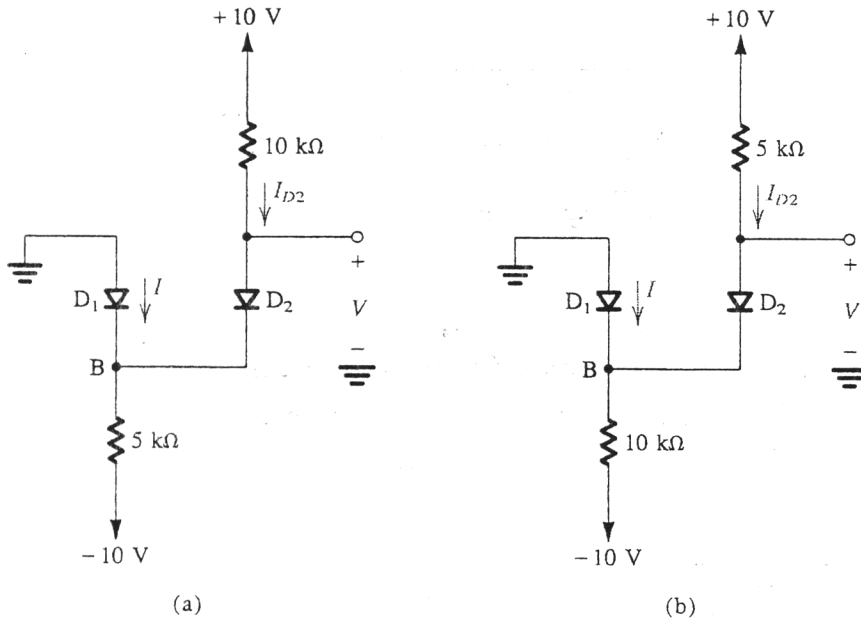


Fig. 2

3. [15%]

For the circuit in the Fig. 3, let  $|V_t| = 2V$ . For each of the cases

- (a)  $K_2 = K_1$  (7%), and
- (b)  $K_2 = 0.01K_1$  (8%), find  $V_o$  corresponding to  $V_i = 0V, 3V,$  and  $6V$ .

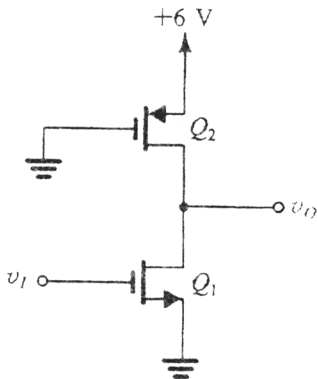


Fig. 3

4. [25%]

The equivalent circuit of an amplifier is shown in Fig. 4. The input signal source is coupled to the amplifier input via coupling capacitor  $C_C$ . Capacitor  $C_L$  represents a parasitic capacitance appearing across the load resistance  $R_L$ .

- (a) Derive an expression for the amplifier voltage gain  $A(s) \equiv V_o(s)/V_i(s)$ . (5%)
- (b) Noting that  $C_C$  is responsible for the frequency dependence of the gain at low frequencies and that  $C_L$  causes the gain to fall off at high frequencies, find the midband gain  $A_M$ ,  $F_L(s)$ , and  $F_H(s)$ . (5%)
- (c) For  $R_s = 10K\Omega$ ,  $R_i = 100K\Omega$ , and  $R_L = 10K\Omega$ , find the required value of  $G_m$  to

注意：背面尚有試題

obtain a midband gain of 20dB. (5%)

- (d) Find the minimum value of  $C_C$  so that  $f_L$  is at most 10Hz. (5%)
- (e) Find the maximum value that  $C_L$  can have while  $f_H$  is at least 1MHz. (5%)

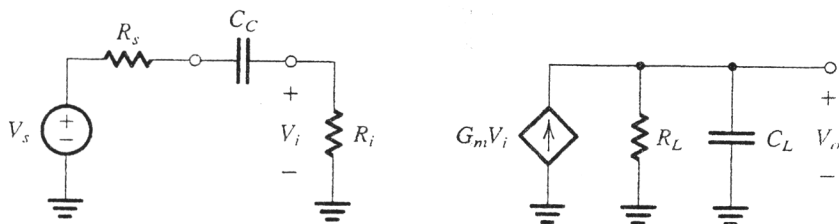


Fig. 4

5. [10%]

For the circuit of Fig. 5, use the feedback method to find the voltage gain  $V_o/V_s$  (4%), the input resistance  $R'_{if}$  (3%), and the output resistance  $R'_{of}$  (3%). The op amp has open loop gain  $\mu = 10^4$  V/V,  $R_{id} = 100K\Omega$ ,  $R_{icm} = \infty$ , and  $r_o = 1K\Omega$ .

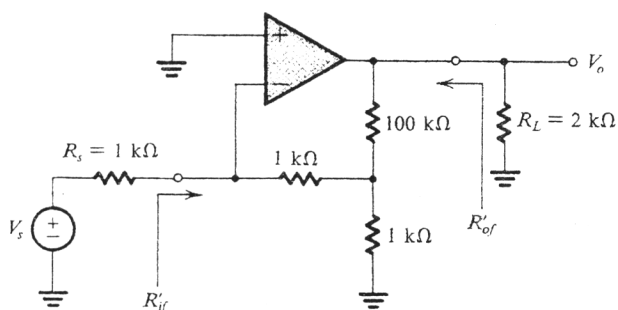


Fig. 5

6. [10%]

Figure 6 shows an enhancement-MOSFET class AB output stage. All transistors have  $|V_t| = 1$  V and  $K_1 = K_2 = nK_3 = nK_4$ . Also,  $K_3 = 1\text{mA/V}^2$ . For  $I_{\text{bias}} = 100\mu\text{A}$  and  $R_L = 1K\Omega$ , find the value of  $n$  that results in a small-signal gain of 0.99 for output voltages around zero, and the corresponding value of  $I_Q$ .

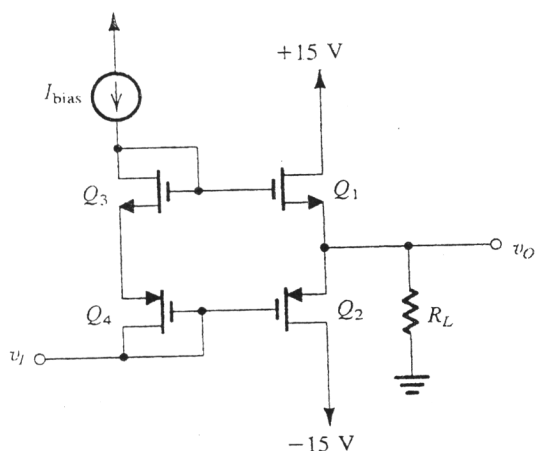


Fig. 6


7. [5%]

A particular transistor having a thermal resistance  $\theta_{JA} = 2^\circ\text{C/W}$  is operating at an ambient temperature of  $30^\circ\text{C}$  with a collector-emitter voltage of 20V. If long life requires a

maximum junction temperature of  $130^{\circ}\text{C}$ , what is the corresponding device power rating? (2%) What is the greatest average collector current that should be considered? (3%)

8. [15%]

Consider the bandpass circuit shown in Fig. 7. Let  $C_1 = C_2 = C$ ,  $R_3 = R$ ,  $R_4 = R/4Q^2$ ,  $CR = 2Q/\omega_0$ , and  $\alpha = 1$ . Disconnect the positive input terminal of the op amp from ground and apply  $V_i$  through a voltage divider  $R_1$ ,  $R_2$  to the positive input terminal. Analyze the circuit to find its transfer function  $V_o/V_i$ . Find the voltage-divider ratio  $R_2/(R_1+R_2)$  so that the circuit realizes (a) an all-pass function (7%), and (b) a notch function. Assume the op amp to be ideal. (8%)

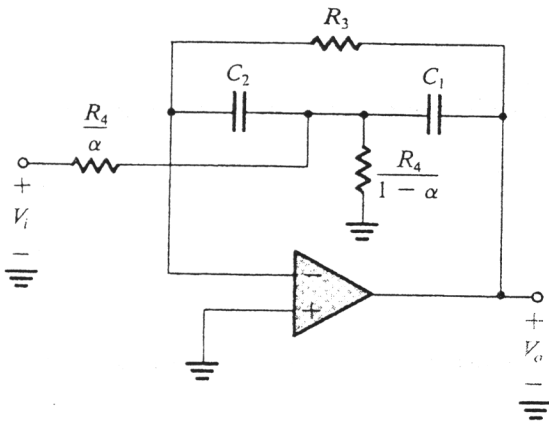

**Fig. 7**