

# 國立臺北科技大學

## 九十三年學年度電腦通訊與控制研究所入學考試

### 電子學（丙組）試題

填准考證號碼

第一頁 共二頁

--	--	--	--	--	--	--	--	--	--

注意事項：

1. 本試題共【六】題，配分共 100 分。
2. 請按順序標明題號作答，不必抄題。
3. 全部答案均須答在答案卷之答案欄內，否則不予計分。

1. For the circuit shown in Fig. P1
  - (a) Derive an expression for the transfer function  $V_o/V_i$ . (6%)
  - (b) Find its input impedance. (6%)
  - (c) Find  $V_o(t)$  as  $V_i(t)=A\cos(\omega t)$ . (3%)

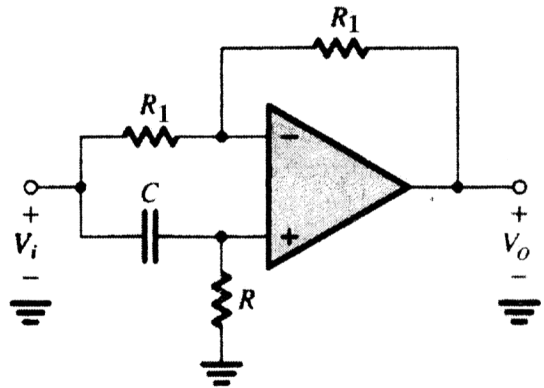


Fig. P1

2. An amplifier has the gain transfer function
 
$$A(s) = 10^2 \frac{s}{s + 2\pi \times 10^2} \frac{1}{1 + s/(2\pi \times 10^5)}$$
  - (a) Sketch a Bode plot for its magnitude, (8%)
  - (b) Find the midband gain, (2%)
  - (c) Find the lower 3-dB frequency  $f_L$ , and the upper 3-dB frequency  $f_H$ . (4%)
  - (d) Find approximate values for the frequencies at which the gain decreases to unity. (6%)

3. Fig. P3.1 is a voltage follower connected by using the general purpose operational amplifier as shown in Fig. P3.2. But the circuit oscillates, i.e., there is a sinusoidal output signal as zero input.
  - (a) What is the cause of the oscillation? (6%)
  - (b) Propose a method to stop the oscillation and explain the reason. (6%)

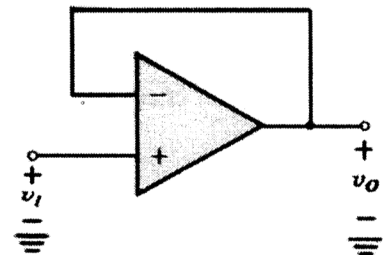


Fig. P3.1

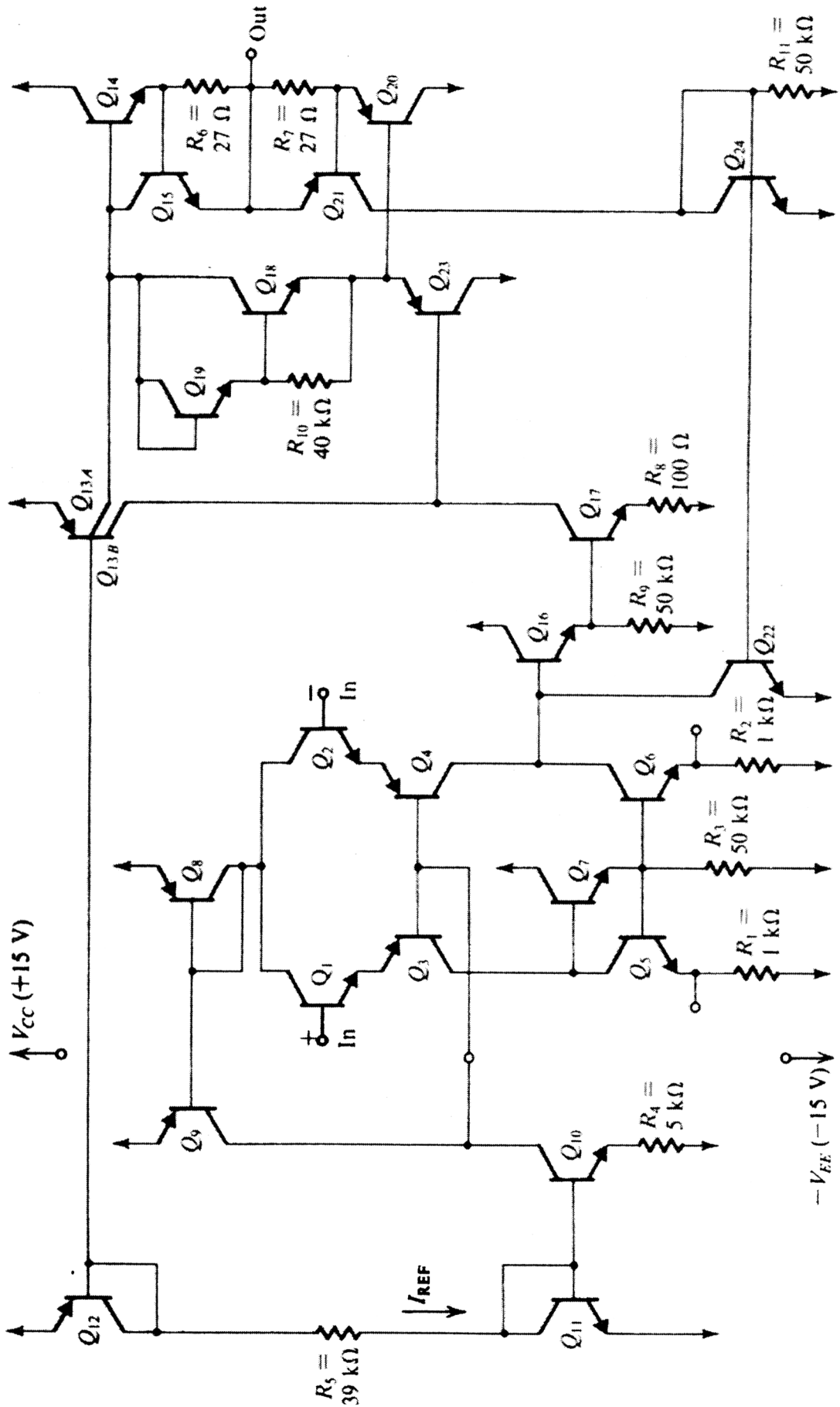


Fig. P3.2

注意：背面尚有試題

4. For the circuit shown in Fig. P4.1, the diodes are assumed to be ideal.
- Describe the transfer characteristic of the circuit. (8%)
  - The circuit is driven by the signal as shown in Fig. P4.2, sketch and label the output waveform. (4%)

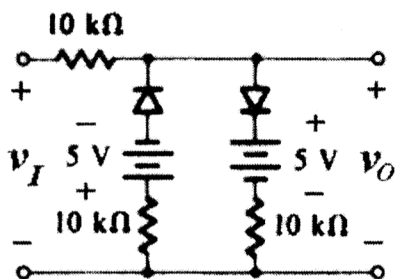


Fig. P4.1

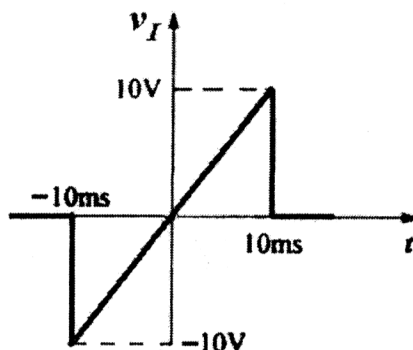


Fig. P4.2

5. For the circuit shown in Fig. P5.1, the diode is assumed to be ideal,  $R_2C \gg T$  and  $R_1C \ll T$ , sketch the output waveform for the input shown as Fig. P5.2. (15%)

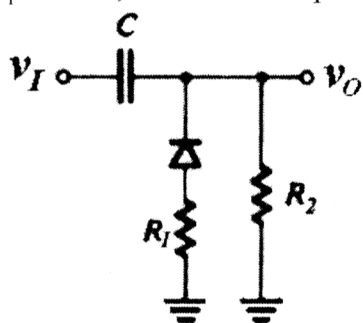


Fig. P5.1

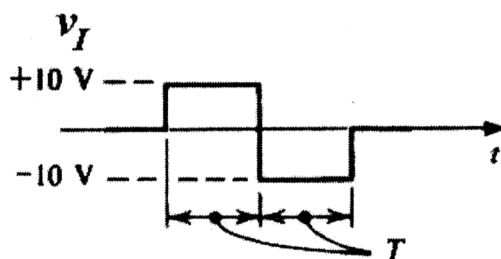


Fig. P5.2

6. Consider the amplifier circuit of Fig. P6 with a bias current  $I = 1$  mA and a collector resistor  $R_C = 5$  k $\Omega$ . Let the BJT have  $\beta = 100$ , and neglect the Early effect. The signal source has a resistance  $R_s = 5$  k $\Omega$ .

- Please sketch the small signal equivalent circuit. (5%)
- Find the value of  $R_e$  that gives the amplifier an input resistance four times that of the source. (5%)
- For the resulting circuit, find voltage gain  $A_v = \frac{v_o}{v_s}$ . (10%)
- If  $v_{\pi}$  is to be limited to 5 mV, find the maximum  $v_s$  that can be applied with and without  $R_e$  included. (6%)

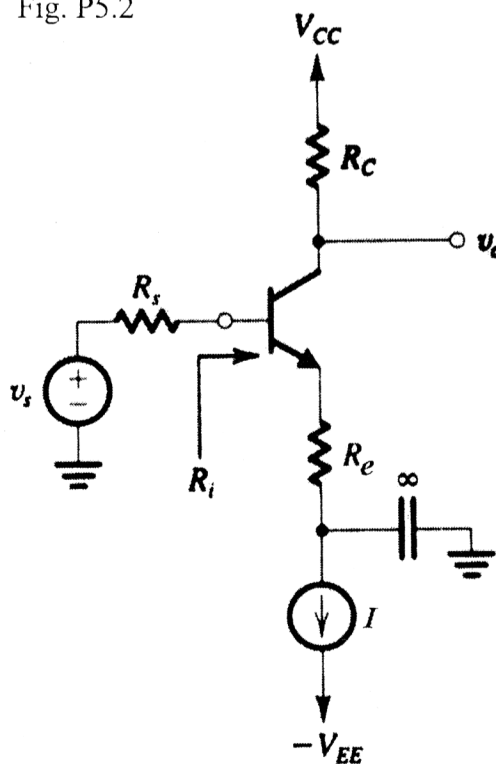


Fig. P6