

國立臺北科技大學

九十四學年度光電工程系碩士班入學考試

電子學試題

填准考證號碼

第一頁 共二頁

--	--	--	--	--	--	--	--

注意事項：

1. 本試題共【7】題，配分共100分。
2. 請按順序標明題號作答，不必抄題。
3. 全部答案均須答在答案卷之答案欄內，否則不予計分。

1. [10%]

For the p-n junction breakdown, the two possible breakdown mechanisms are the zener effect (5%) and the avalanche effect (5%). Please briefly describe them.

2. [15%]

A silicon (energy gap = 1.12eV) abrupt p-n junction in thermal equilibrium at T = 300K is doped such that $E_C - E_F = 0.21\text{eV}$ in the n region and $E_F - E_V = 0.18\text{eV}$ in the p region (see the Fig. 1). ($n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$, $E_i \cong E_{\text{midgap}}$, $\epsilon_s = 11.9 \times 8.854 \times 10^{-14} \text{ F/cm}$)

- (a) Determine the impurity doping concentrations in each region. (5%)
- (b) Determine the built-in voltage V_{bi} . (5%)
- (c) Determine the depletion width. (5%)

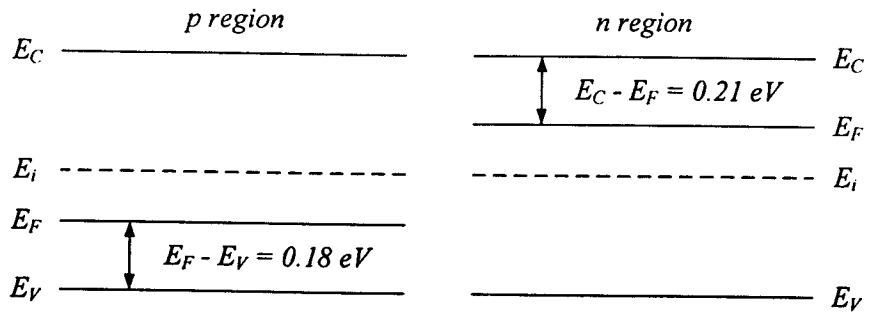


Fig. 1

3. [15%]

In the circuit shown in the Fig. 2, v_s is a small sine-wave signal with zero average value.

Assume $\beta = 50$,

- (a) Find R_{in} . (5%)
- (b) Find v_o/v_s . (5%)
- (c) If the amplitude of the signal v_{be} is limited to 5mV, what is the largest signal at the input? (5%)

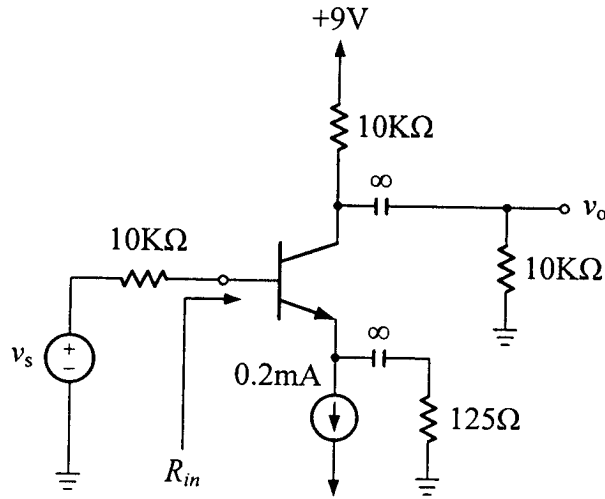


Fig. 2

4. [15%]

Consider the circuit shown in the Fig. 3. Assume $C_{gd} = 1\text{pF}$, $C_{gs} = 4\text{pF}$, $g_m = 5\text{mA/V}$ (both FETs have the same bias current), $R_s = 2\text{K}\Omega$ and $R_L = 3\text{K}\Omega$.

- (a) Find the midband voltage gain v_X/v_Y . (5%)
- (b) Find the over-all midband voltage gain v_o/v_s . (5%)
- (c) Please estimate the bandwidth of this circuit. (5%)

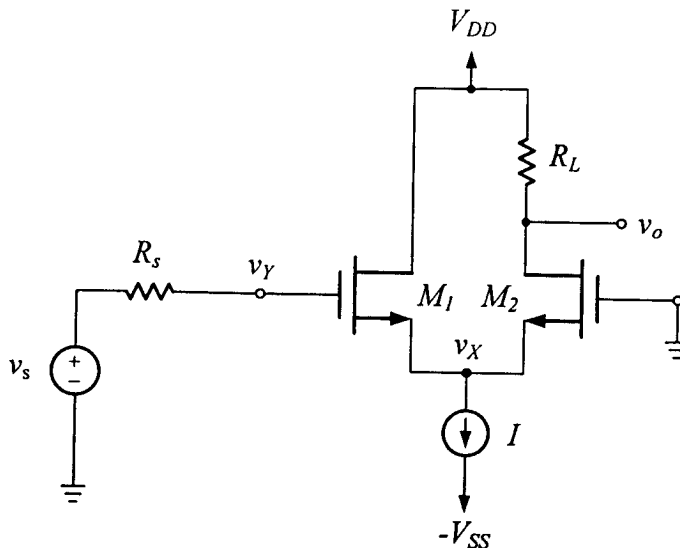


Fig. 3

5. [20%]

As shown in the Fig. 4, the circuit is composed of three gain stages with feedback provided by the network composed of R_{E1} , R_F , and R_{E2} . Assume that the bias circuit causes $I_{C1} = 2.5\text{mA}$, $I_{C2} = 2.5\text{mA}$, and $I_{C3} = 0.5\text{mA}$. Using these values and assuming $h_{fe} = 100$ and $r_o = \infty$, find:

- (a) the open-loop gain A , (4%)
- (b) the feedback factor β , (4%)
- (c) the voltage gain V_o/V_s , (4%)
- (d) the input resistance R_{in} , (4%) and
- (e) the output resistance R_{of} . (4%)

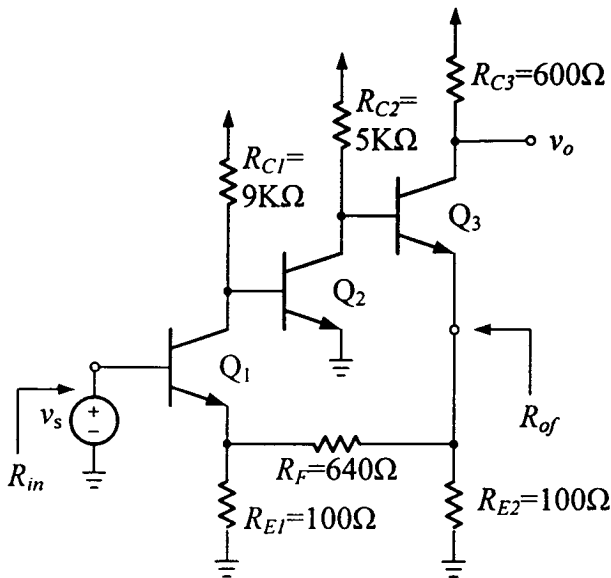


Fig. 4

6. [10%]

Consider the circuit in the Fig. 5, in which $R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = 10\text{K}\Omega$, $V_{DD} = 5\text{V}$, and $V_I = 3\text{V}$.

- (a) Assume the op amp have infinite gain. What are the values of current I_1 and I_2 ? (5%)
- (b) Find the current I_1 and I_2 again using op amps with a finite gain ($A=10$) for the same circuit. (5%)

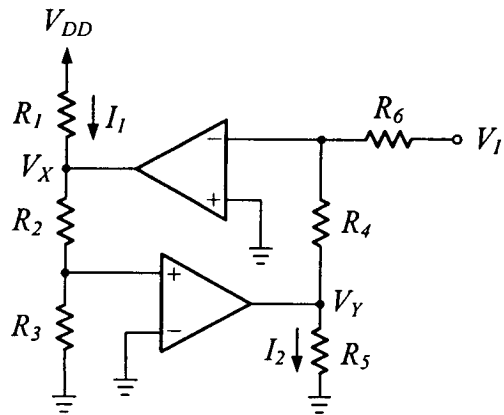


Fig. 5

7. [15%]

A pass-transistor logic circuit is shown in the Fig. 6. Determine the truth table for this circuit. (10%) What logic function does it implement? (5%)

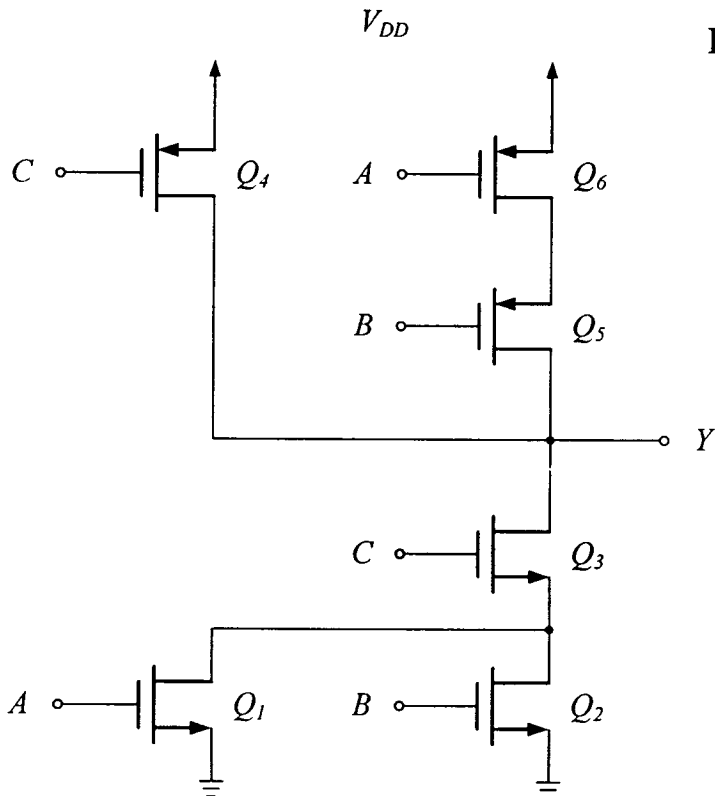


Fig. 6