

## 國立臺北科技大學九十五學年度碩士班招生考試

系所組別：1740 電腦與通訊研究所丁組

## 第二節 電子學 試題

填准考證號碼

--	--	--	--	--	--	--	--

第一頁 共二頁

**注意事項：**

1. 本試題共 10 題，配分共 100 分。每題 10 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

1. The CMOS layout is shown in Fig.1, sketch the corresponding CMOS circuit and what function is provided for this circuit ?

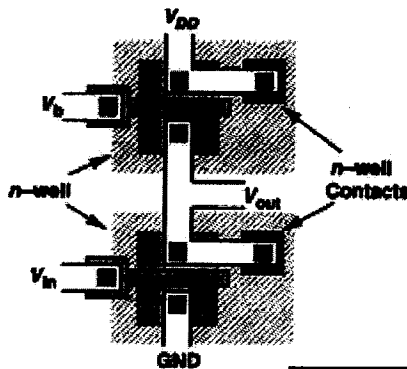


Fig.1

2. In the Fig.2, assume that the transconductance and output resistance of nMOS are  $g_{mN}$  and  $r_{oN}$ . The transconductance and output resistance of pMOS are  $g_{mP}$  and  $r_{oP}$ . Find the small-signal differential gain  $V_{out}/V_{in}$ .

 


Fig.2

3. In the Fig.3, assume that the transconductances of all MOS are  $g_m$  and output resistances of all MOS are infinite.  $C_{GS1}$ ,  $C_{GS2}$ ,  $C_{GD1}$ ,  $C_{GD2}$ ,  $C_{DB1}$ ,  $C_{DB2}$  and  $C_{SB2}$  are the equivalent capacitances of MOS high frequency model.  $C_L$  is load capacitance. Use Miller effect to find the three poles of node A, node X and node Y.

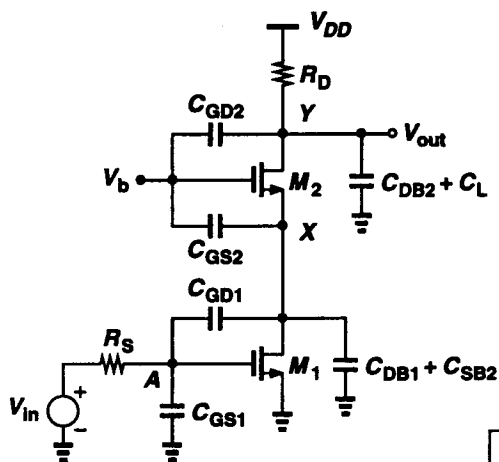


Fig.3

4. In the Fig.4, what type of feedback is used for this circuit ? Assume that the transconductances of MOS are  $g_m$  and output resistance is infinite, find the voltage gain  $V_{out}/V_{in}$

 


Fig.4

5. In the Fig.5, the closed-loop voltage gain is equal to 10, find the minimum value of  $A_1$  for a gain error of 1%.

 


Fig.5

注意：背面尚有試題

6. In the Fig.6, the input signal is  $V_i$ , sketch the corresponding block-diagram realization and what functions are provided for the three output voltages in this circuit ?

 


Fig.6

7. In the Fig.7,  $v_A$  is assumed to be negative, what function is provided for this circuit and explain the operation principle.

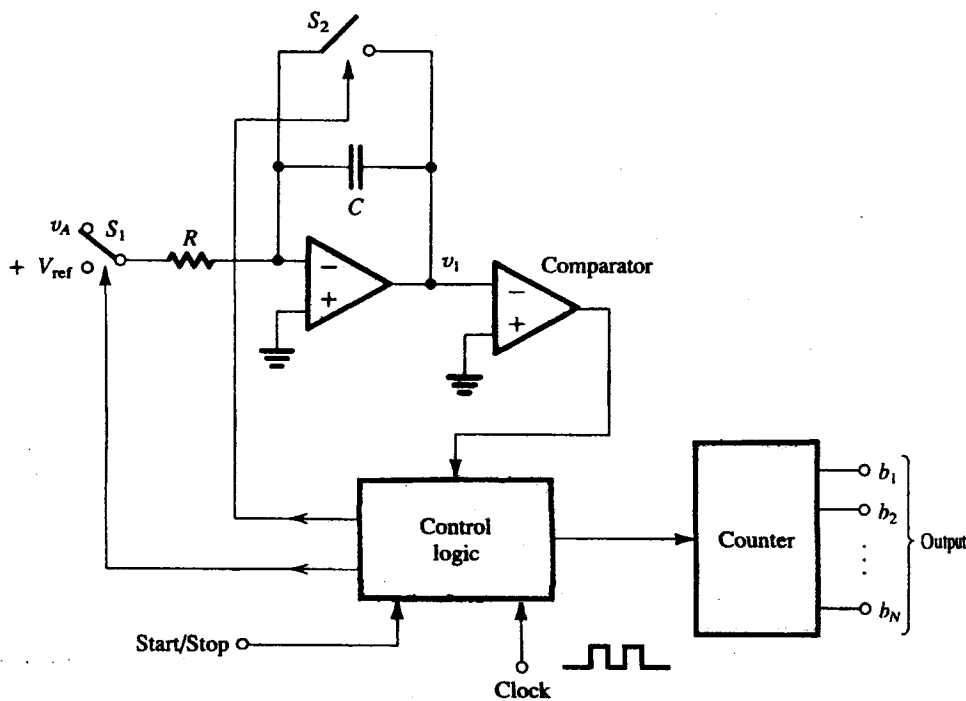


Fig.7

8. In the Fig.8, what function is provided for the  $V_o$  in the circuit ? Explain it clearly.

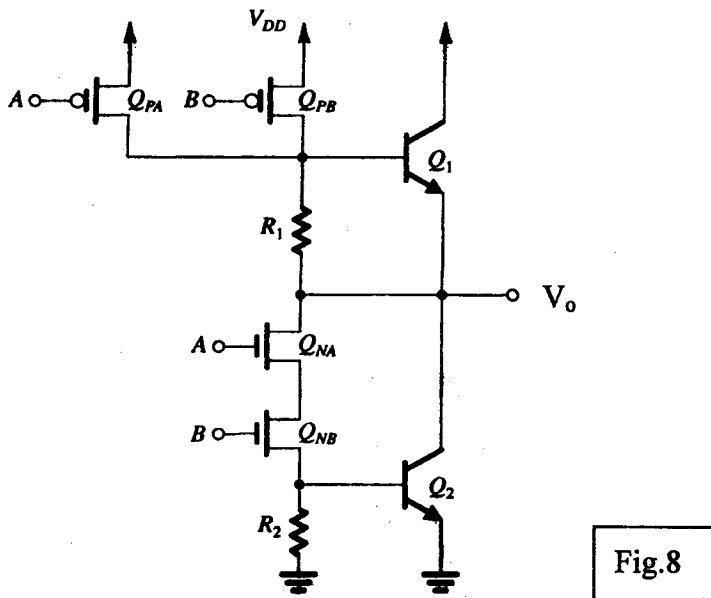


Fig.8

9. In the Fig.9,  $\phi$  is clock, what function is provided for the  $V_o$  in the circuit ? Explain it clearly.

 


Fig.9

10. Given inputs  $A, B, C, D, E$ , design a CMOS logic circuit to implement the logic function  $Y = (A+B)(C+D)E$ .