

# 國立臺北科技大學九十五學年度碩士班招生考試

系所組別：1111 機電整合研究所甲組

## 第二節 電子學（選考）試題

填准考證號碼


--	--	--	--	--	--	--	--

第一頁 共二頁

### 注意事項：

1. 本試題共 4 大題，第 1 大題為填充題共 60 分，第 2、3、4 大題分別為 10、15、15 分，共 100 分。
2. 請按順序標明題號作答，不必抄題，數值答案請提供四位有效數字。
3. 全部答案均須答在答案卷之答案欄內，否則不予計分。

1. To each of the blanks below, please sequentially put your answers on your answer sheet.  
(@6%\*10=60%)

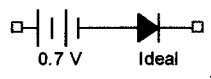- (1) If each of the diodes in Fig. 1 can be equivalently expressed as , then the current through diode  $D_2$  should be 1.1 mA.

 


Fig. 1

- (2) To the transistor in Fig. 2, the accurate voltage of operating point (or say Q-point),  $V_{CEQ}$ , should be 1.2 V. The accurate input impedance,  $Z_i$ , of the circuit should be 1.3 kΩ.


 


Fig. 2

 
(3) To the transistor in Fig. 3, the accurate drain current of operating point (or say Q-point),  $I_{DQ}$ , should be 1.4 mA. The accurate voltage gain,  $A_v$ , of the circuit should be 1.5.



- $V_{DD}=40\text{ V}$
- $R_1=22\text{ M}\Omega$
- $R_2=18\text{ M}\Omega$
- $R_D=3\text{ k}\Omega$
- $R_S=0.82\text{ k}\Omega$
- $V_{GS(th)}=5\text{ V}$
- $I_{D(on)}=3\text{ mA at }V_{GS(on)}=10\text{ V}$
- $y_{os}=20\text{ }\mu\text{ S (output admittance)}$

Fig. 3

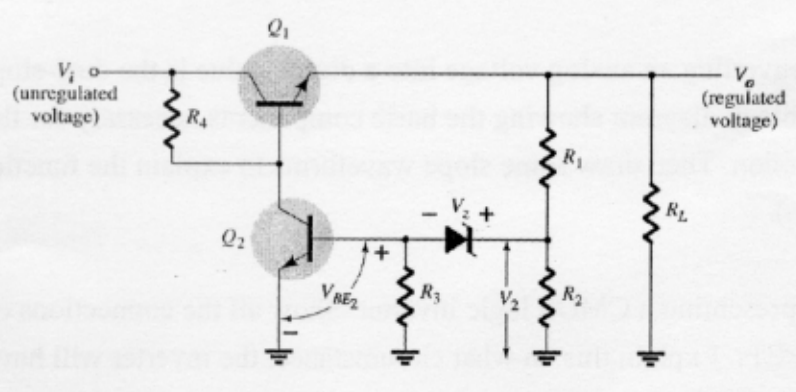(4) For the circuit in Fig. 4, the regulated voltage,  $V_o$ , should be 1.6 V.



- $R_1=20\text{ k}\Omega$
- $R_2=30\text{ k}\Omega$
- $R_3=30\text{ k}\Omega$
- $R_4=10\text{ k}\Omega$
- $V_z=8.3\text{ V}$

Fig. 4

注意：背面尚有試題

met-3

(5) For the active filter shown in Fig. 5, the cutoff frequency should be 1.7 kHz and the voltage gain should be 1.8.

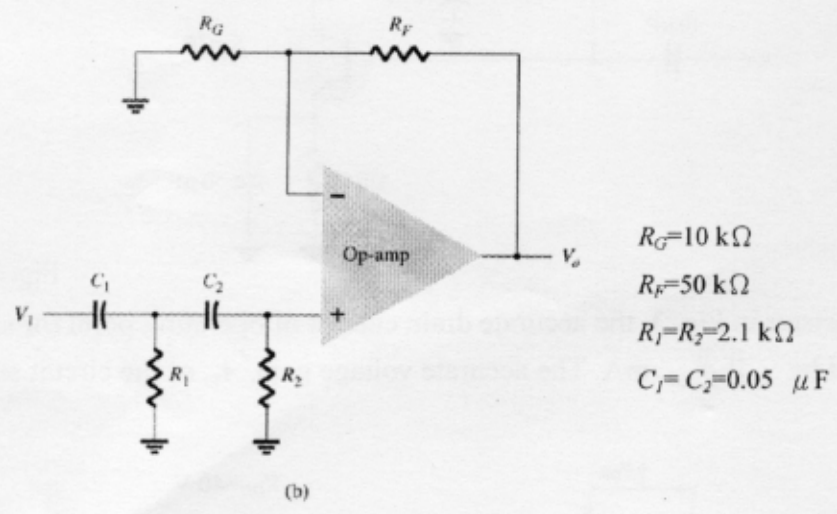


Fig. 5

- (6) Let  $\eta_A, \eta_{A+T}$  and  $\eta_B$  represent the maximal possible efficiency of power amplifiers of class A, transformer-coupled class A and class B respectively. Starting from the highest value to the lowest, their sequence should be 1.9 (For example  $\eta_A > \eta_{A+T} > \eta_B$ ).
- (7) A p-n junction is formed with p region having  $N_a=10^{16} \text{ cm}^{-3}$  and n region having  $N_d=10^{17} \text{ cm}^{-3}$ . At  $27^\circ\text{C}$  (thermal voltage  $V_T=0.026 \text{ V}$ , intrinsic concentration  $n_i=1.5 \times 10^{16} \text{ cm}^{-3}$ ), the build-in potential of the junction's depletion should be 1.10 V.

2. If a diode's current can be expressed as  $I_D = I_S(e^{11600V_D/T} - 1)$ , please prove that the dynamic resistance  $r_d$  can be expressed as  $r_d \cong \frac{26mV}{I_D}$  providing that  $I_D \gg I_S, V_D > 0.7 \text{ V}$  and  $T=300 \text{ }^\circ\text{K}$  (10%).

3. A popular method of converting an analog voltage into a digital value is the dual-slope method. Please draw a block diagram showing the basic components necessary for the analog-to-digital conversion. Then draw some slope waveforms to explain the functions of the block diagram (15%).

4. Please draw a circuit representing a CMOS logic inverter. Show all the connections of each terminal on MOSFETs. Explain this: at what circumstance, the inverter will have a short circuit current and what factors involve in this unwanted situation (15%).