)-

國立臺北科技大學產業研發碩士專班 96 年度秋季班招生考試 系所組別:110 電子電腦與通訊產業研發碩士專班 第一節 電子學 試題

第一頁 共一頁

## 注意事項:

- 1. 本試題共5題,配分共100分。
- 2. 請標明大題、子題編號作答,不必抄題。
- 3. 全部答案均須在答案卷之答案欄內作答,否則不予計分。
- 1. The operational transconductance amplifier (OTA) is a voltage-input current-output active device with the output current  $I_0$ =Gm( $V_+$ - $V_-$ ), where Gm is the transconductance of the OTA,  $V_+$  and  $V_-$  are the voltages of positive and negative terminals of the OTA. If  $V_i$  is the input and  $V_L$  and  $V_B$  are the outputs, find the transfer functions of  $V_B/V_i$  and  $V_L/V_i$  in the following second-order filter shown in Fig.1. (20 %)

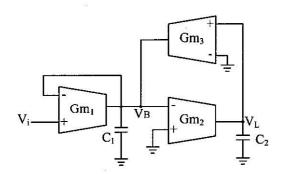


Fig.1

- 2. (a) Sketch the complete small-signal model of MOS transistor including the parasitic capacitors. (10 分)
  - (b) Sketch the cross-section diagram of a CMOS p-well technology. (10 分)
  - (c) What are the second-order effects of MOS transistor? Please explain them clearly. (10 分)

1-2

3. If the transconductances of  $M_1$ ,  $M_2$  and  $M_3$  are  $g_{m1}$ ,  $g_{m2}$  and  $g_{m3}$ , and the output resistances of  $M_1$ ,  $M_2$  and  $M_3$  are  $r_{o1}$ ,  $r_{o2}$  and  $r_{o3}$ , respectively, find the output resistance  $R_{out}$  of the triple cascade circuit shown in Fig.2. (10 %)


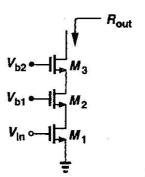


Fig.2

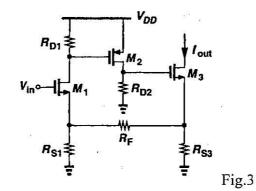4. Neglecting the channel length modulation effect and the body effect, and assume that the transconductances of all MOS transistors are  $g_m$ , find the closed loop gain  $I_{out}/V_{in}$  shown in the Fig.3. (20  $\frac{1}{27}$ )



5. Sketch the block diagram of the dual-slope analog to digital converter and explain the operational principle.  $(20 \, \hat{A})$