

國立臺北科技大學產業研發碩士專班 96 年度秋季班招生考試

系所組別：120 電力電子產業研發碩士專班


第一節 基本電學 試題

第一頁 共一頁


注意事項：

1. 本試題共 5 題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

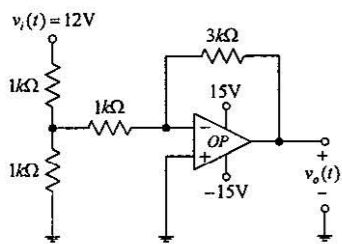1. Find $v_o(t)$ in the following individual circuits. (10%, 10%)




(a)

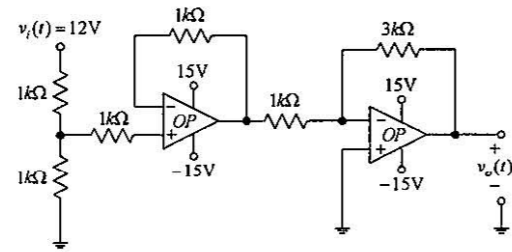


(b)

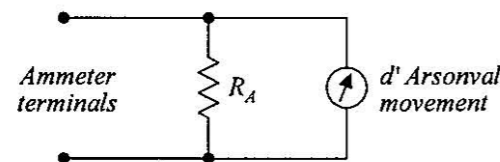2. (a) A 50mV, 1mA d'Arsonval movement is to be used in an ammeter with a full-scale reading of 10mA. Determine R_A . (10%)



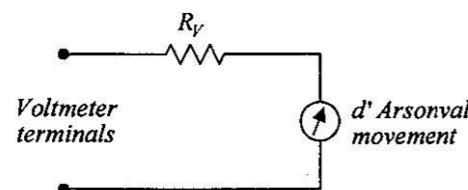
- (b) A 50mV, 1mA d'Arsonval movement is to be used in a voltmeter with a full-scale reading of 5V. Determine R_V . (10%)



3. (a) If the voltage across the device is $v(t) = 5 + 10\sin(\omega t + 30^\circ) + 15\sin(2\omega t + 90^\circ) + 20\sin(3\omega t + 180^\circ)$ V, and the current flowing through the device is $i(t) = 10 + 20\cos\omega t + 30\cos 2\omega t + 40\cos 3\omega t$ A. Determine the power dissipated in this device. (10%)

- (b) A $\frac{480}{\sqrt{3}}$ V_{rms} line feeds two balanced three-phase loads. If two loads are rated as follows.
 Load 1: $5\sqrt{5}$ kVA at 0.8pf, lagging
 Load 2: $10\sqrt{5}$ kVA at 0.6pf, leading
 Determine the magnitude of the line current from the $\frac{480}{\sqrt{3}}$ V_{rms} source. (10%)

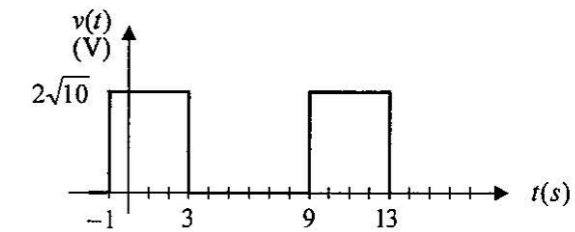4. Find the rms value of the following periodic waveform $v(t)$. (20%)



5. The two parallel inductors in the following circuit are connected across the terminals of a black box at $t = 0$. The resulting voltage $v(t)$ for $t > 0$ is known to be $12e^{-t}$ V. It is also known that $i_1(0) = 2$ A and $i_2(0) = 4$ A. How much energy is trapped in the two inductors? (20%)

