

第一節 電子學 試題

第一頁 共三頁

注意事項：

1. 本試題共五題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

一、Assume the operational amplifiers are ideal.

1. For the circuit shown in Fig. 1(a), Find the Z_i .(10%)

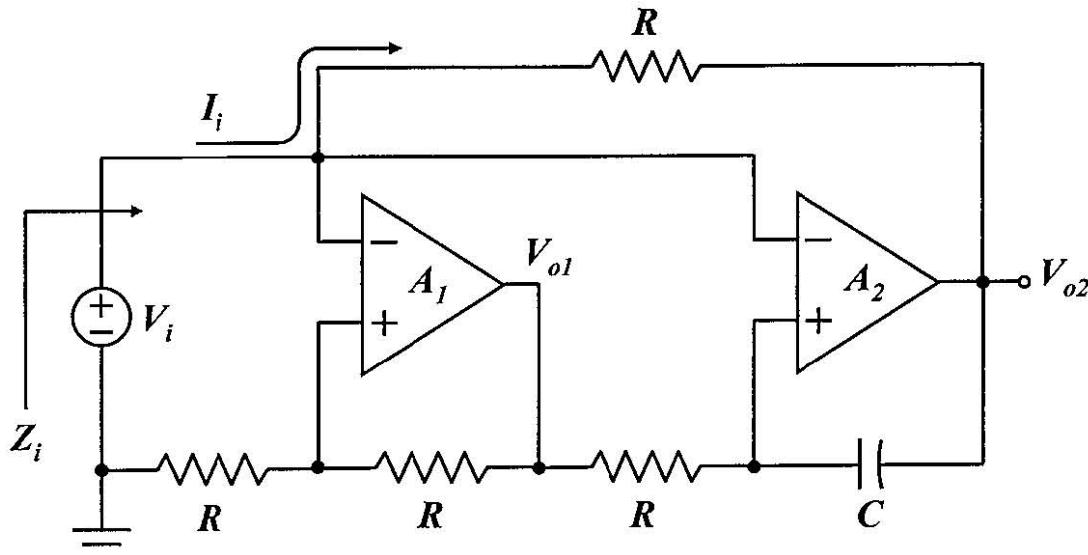


Fig. 1(a)

2. For the circuit shown in Fig. 1(b), Find the Z_{in} .(10%)

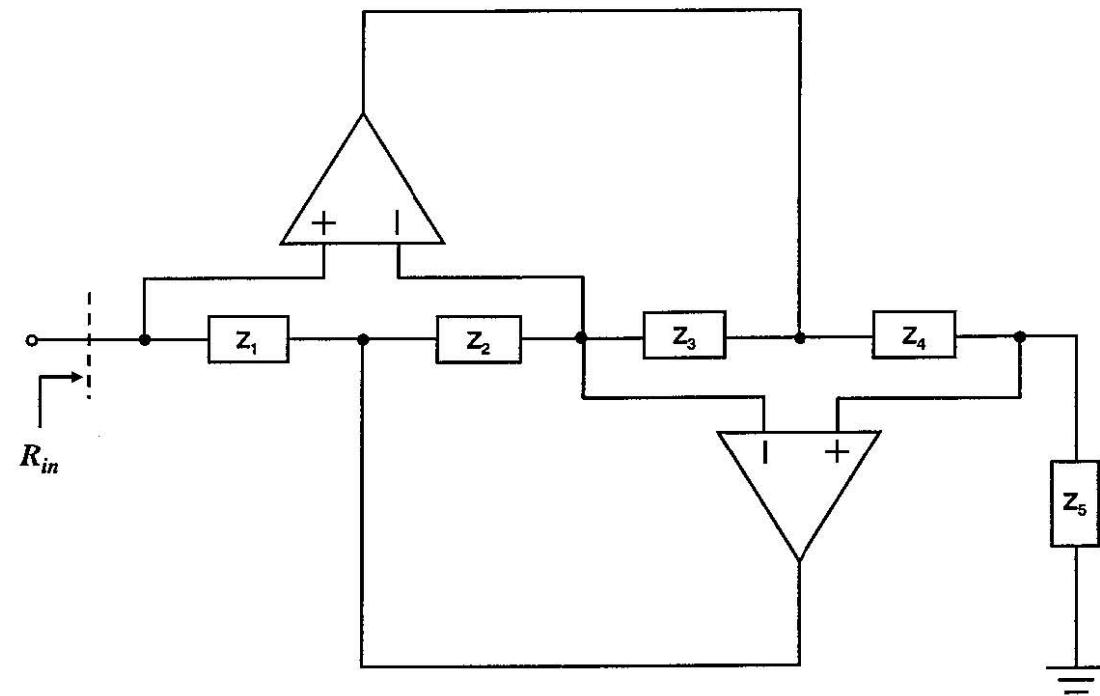


Fig. 1(b)

二、Assume the operational amplifiers are ideal.

1. For the circuit shown in Fig. 2(a), Find and plot the transfer characteristic V_o as a function of V_i .(5%)

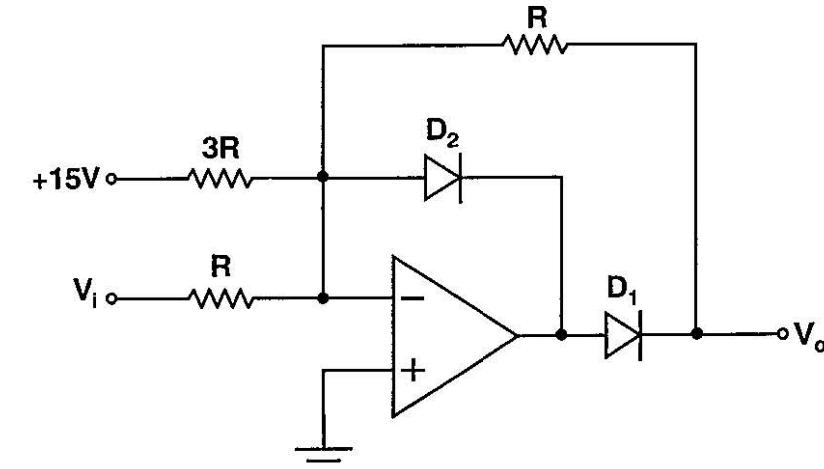


Fig. 2(a)

注意：背面尚有試題

4 - 3

2. For the circuit shown in Fig. 2(b), Find the V_o . (5%)

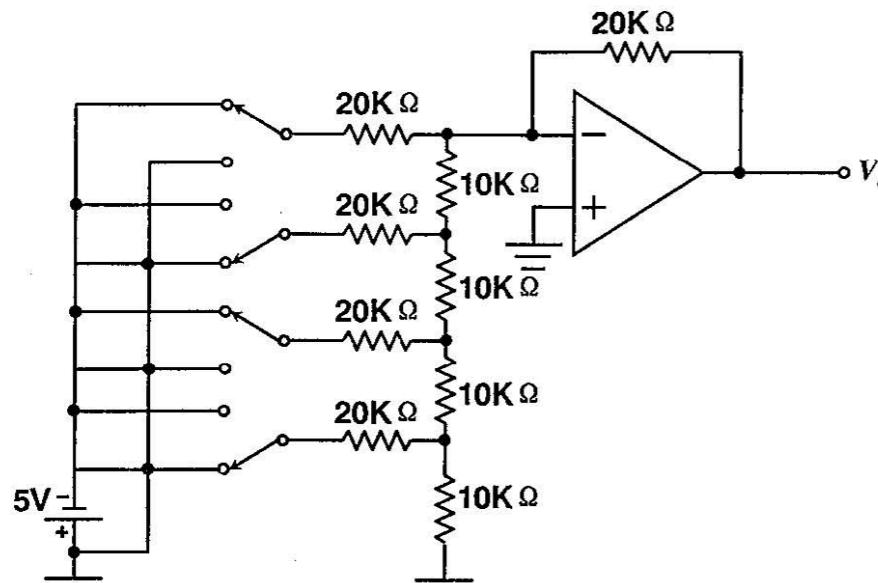


Fig. 2(b)

3. For the circuit shown in Fig. 2(c), find the voltage of X. (5%)

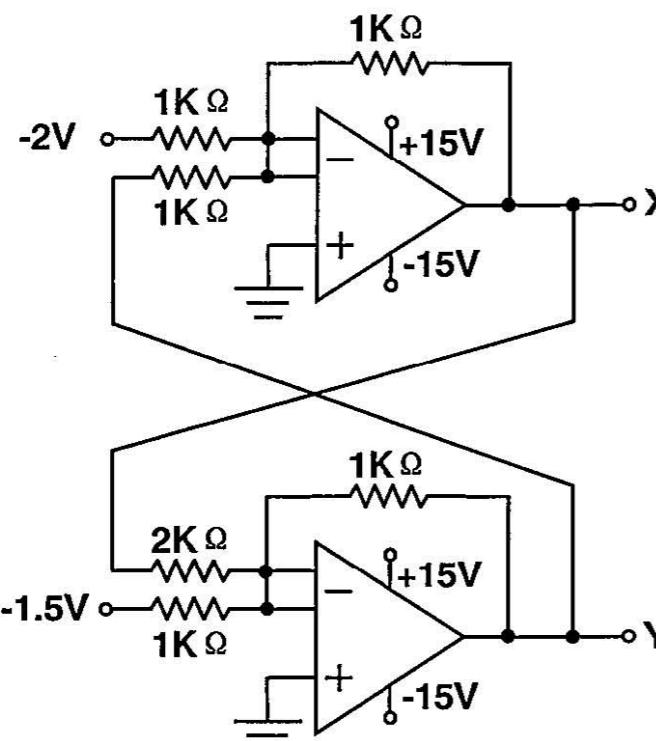


Fig. 2(c)

4. For the circuit shown in Fig. 2(d), find the I_o . (5%)


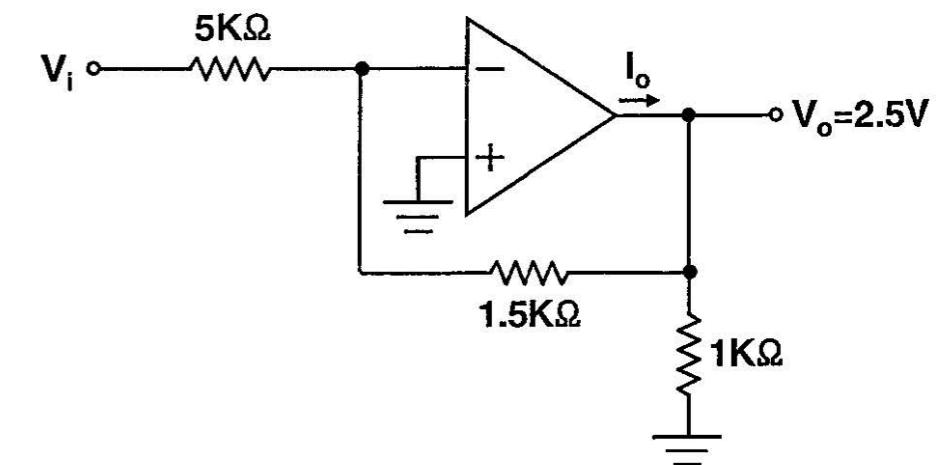


Fig. 2(d)

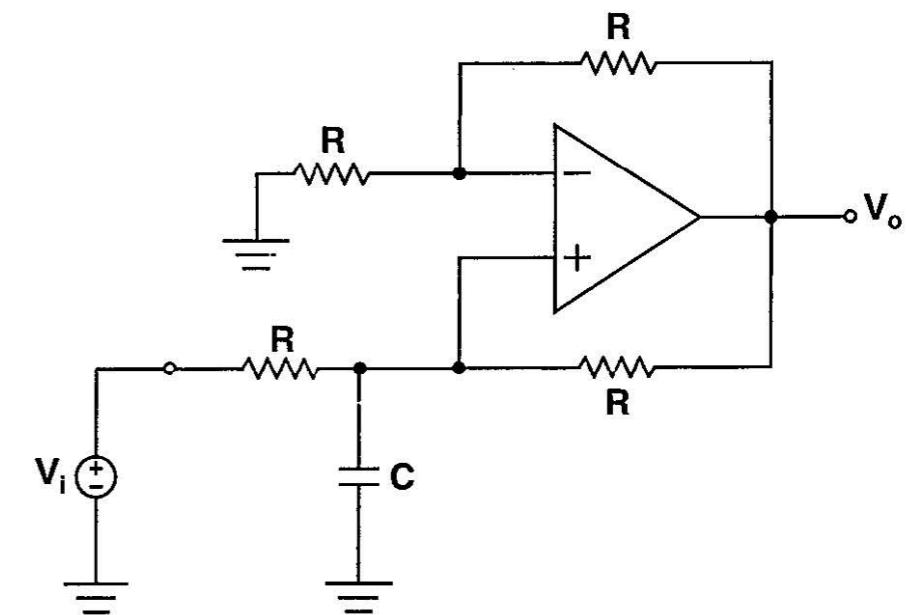三、For the circuit shown below, assume the operational amplifiers are ideal.



1. Prove the $\frac{V_o}{V_i} = \frac{2}{sRC}$. (10%)


2. Design two different circuits to satisfy the $\frac{V_o}{V_i} = \frac{2}{sRC}$

(1) Use two operational amplifiers. (5%)

(2) Only use one operational amplifier. (5%)

四、For the circuit shown below, Calculate the $\frac{v_o}{v_s}$. ($\beta = 100$, $R_F = 100k\Omega$, $R_E = 1k\Omega$,

$R_L = 100k\Omega$, $I = 1mA$) (20%)

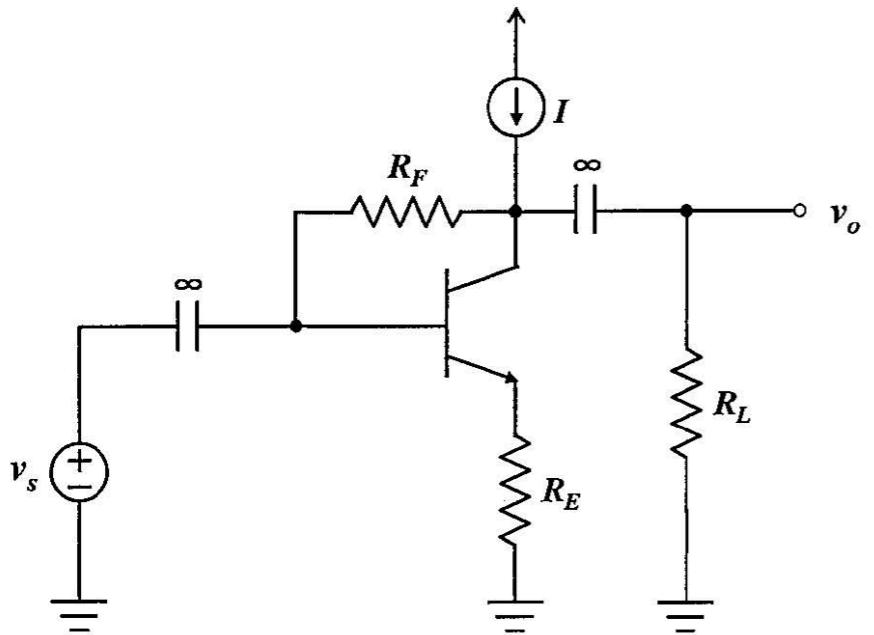

五、For the circuit shown below, find R_{in} , R_{out} and A_v . (20%)

