

國立臺北科技大學九十六學年度碩士班招生考試

系所組別：1740 電腦與通訊研究所丁組

第二節 電子學 試題

第一頁 共二頁

注意事項：

1. 本試題共 10 題，配分共 100 分。每題 10 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

1. Use only one operational amplifier to design a circuit with the following output $V_o(s)$, where $V_1(s)$ and $V_2(s)$ are the inputs.

$$V_o(s) = -\frac{1}{8s}V_1(s) + \frac{1}{4}\left(1 + \frac{1}{8s}\right)V_2(s)$$

2. The operational transconductance amplifier (OTA) is a voltage-input current-output active device with infinite input impedances and the output current $I_o = g_m(V_+ - V_-)$, where g_m is the transconductance of the OTA, V_+ and V_- are the voltages of positive and negative terminals of the OTA. If $g_{m1} = g_{m2} = g_{m3} = g_m$, and V_1, V_2, V_3, V_4 are the inputs and V_{o1}, V_{o2}, V_{o3} are the outputs, find the pole frequency ω_o and quality factor Q of the biquadratic filter shown in Fig.1.

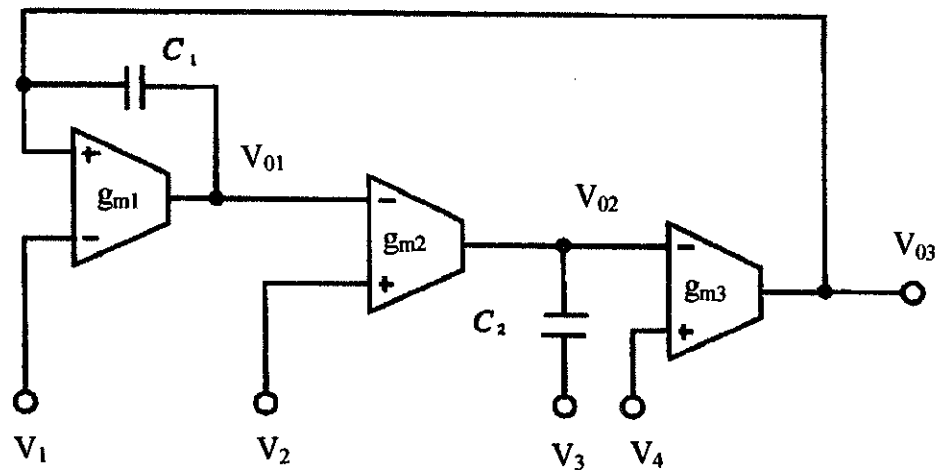


Fig.1

3. The second-generation current conveyor (CCII) is a new active device with the following relationships: $I_Y = 0, V_X = V_Y, I_Z = \pm I_X$, where plus and minus signs denote CCII+ and CCII-, respectively. The plus sign is taken to mean I_X and I_Z both flowing simultaneously toward or away from the CCII+, and the minus sign indicates I_X flowing into the CCII- and I_Z flowing out the CCII-, and vice versa. Find the condition of oscillation and the frequency of oscillation of the oscillator shown in Fig.2.

 


Fig.2

4. A CMOS double pair is shown in Fig.3, where both MOS transistors are in the saturation region. The transistor pair can be equivalent to a single transistor with an equivalent threshold voltage V_{t-eq} and equivalent device parameter K_{eq} . We define the equivalent threshold voltage V_{t-eq} as $V_{t-eq} = V_{tn} - V_{tp}$, where V_{tn} and V_{tp} are the threshold voltages of NMOS Q_n and PMOS Q_p , and $V_{tn} > 0, V_{tp} < 0$. If K_n and K_p are the device parameters of Q_n and Q_p , find the equivalent device parameter K_{eq} using K_n and K_p .

 


Fig.3

5. The fastest analog-to-digital converter (ADC) is called the simultaneous, parallel or flash ADC. Sketch the circuit of a 3-bit flash ADC.

注意：背面尚有試題

enb-3

6. Fig.4 shows the basic two-stage CMOS operational amplifier. Explain the operating principle of the circuit including the function of every element clearly and what are the advantages and disadvantages of the two-stage CMOS operational amplifier?

 


Fig.4

7. In the Fig.5, what type of feedback circuit is employed in the current amplifier? Neglect the channel length modulation effect and the body effect and assume that the transconductances of all MOS transistors are g_m , find the current gain I_{out}/I_{in} .

 


Fig.5

enb-6

8. Given six inputs A, B, C, D, E, F, design a Domino CMOS logic circuit to implement the logic function $Y = AB + C + DEF$.

9. Fig.6 shows the CMOS layout, sketch the corresponding CMOS circuit, where a, b, c are three inputs, and Out is the output.

 


Fig.6

10. Sketch the cross-section diagram and the I_D - V_{GS} characteristic curve of a double-diffused vertical power MOS transistor (DMOS).