

國立臺北科技大學九十七學年度碩士班招生考試

系所組別：1111 機電整合研究所甲組

第二節 電子學 (選考) 試題

填准考證號碼

--	--	--	--	--	--	--	--	--	--

第一頁 共二頁

注意事項：

1. 本試題共 5 題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

1. (a) Explain the Ohm's Law and Kirchhoff's Voltage Law (5%)

(b) Determine the total current through the circuit in Fig. 1 (If ideal diode can be equivalently express as $0.7V$ Ideal) (5%)

equivalently express as $0.7V$ Ideal (5%)

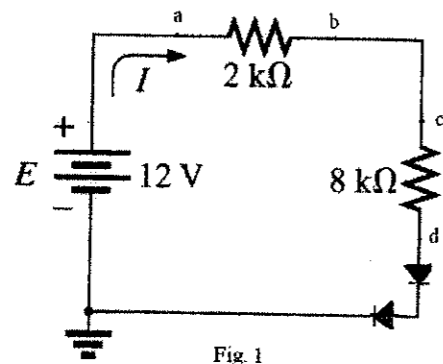


Fig. 1

(c) Determine the V_{ab} and V_{cd} (voltage drop between points a and b) as shown in Fig. 1 (5%)

2. A series R-C circuit as shown in Fig. 2, the values of E, R, and C are 40V, 8KΩ and 4 μF respectively. Answer the following questions

- (a) Determine the time constant τ (3%)
- (b) Find the mathematical equation for the transient behavior of V_c , i_c and V_R (10%)
- (c) Plot the waveform of V_c versus time. (6%)
- (d) What is the value of V_c at $t=20ms$? (3%)
- (e) On the practical basis, how much time pass before we can assume that the charging phase has passed. (3%)

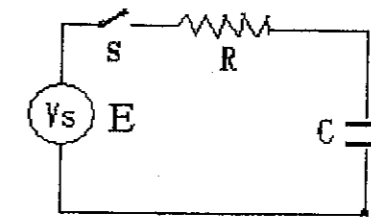


Fig. 2

3. An On-Off control circuit (Schmitt trigger) is shown in Figure 3.

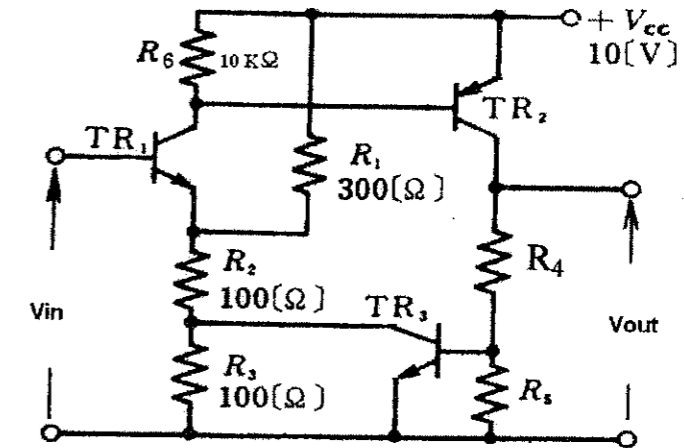


Fig. 3

- (a) If input voltage is $V_{in}=3V$, determine the voltage V_{R1} , V_{R2} , V_{R3} , V_{R4} , V_{R5} (10%)
- (b) If input voltage is $V_{in}=6V$, determine the voltage V_{R1} , V_{R2} , V_{R3} , V_{R6} , V_{out} (10%)
(V_{R1} : voltage drop of resistance R_1)

4. Assume that the C nod point is ground point ($V_c=0$) as shown in figure 4,

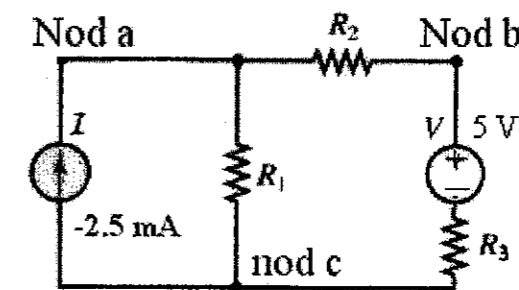


Fig. 4

- (a) Find the mathematical nod equation for points a and b (10%)
- (b) Determine the voltage of V_{ac} , V_{bc} , V_{R1} , V_{R2} , and V_{R3} (10%)
($I=-2.5mA$, $V=5V$, $R_1=1K\Omega$, $R_2=2K\Omega$, $R_3=3K\Omega$)

5. For the transistor configuration in Fig. 5 in which V_{BE} have been provide as $V_{BE}=0.7V$, answer the following questions: (20%)

- (a) Determine the voltage V_E and the current I_E (5%)

- (b) Calculate V_{R1} (5%)
- (c) Determine V_{RC} using the fact that the approximation $I_C = I_E$ is often applied on transistor network (5%)
- (d) Calculate the V_{CE} and $V_{C-ground}$ (5%)

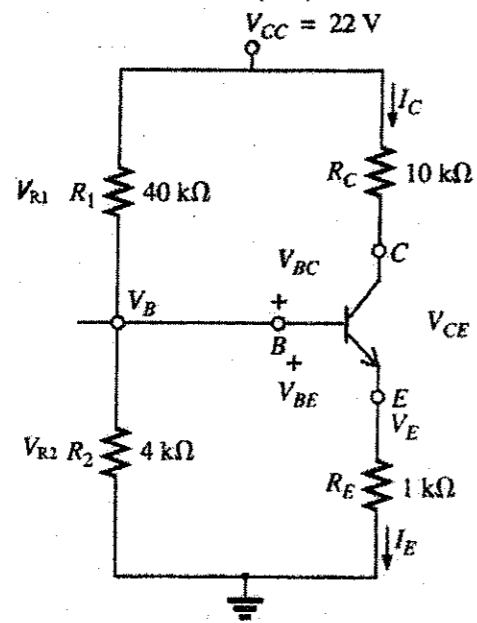


Fig. 5