

111 電子學 試題

填准考證號碼

--	--	--	--	--	--

第一頁，共三頁

**注意事項：**

1. 本試題共 5 題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

一、Using the simple constant-voltage-drop (0.7V) for each of the diodes, find the transfer characteristic of the circuit shown in Fig. 1. (20 分)

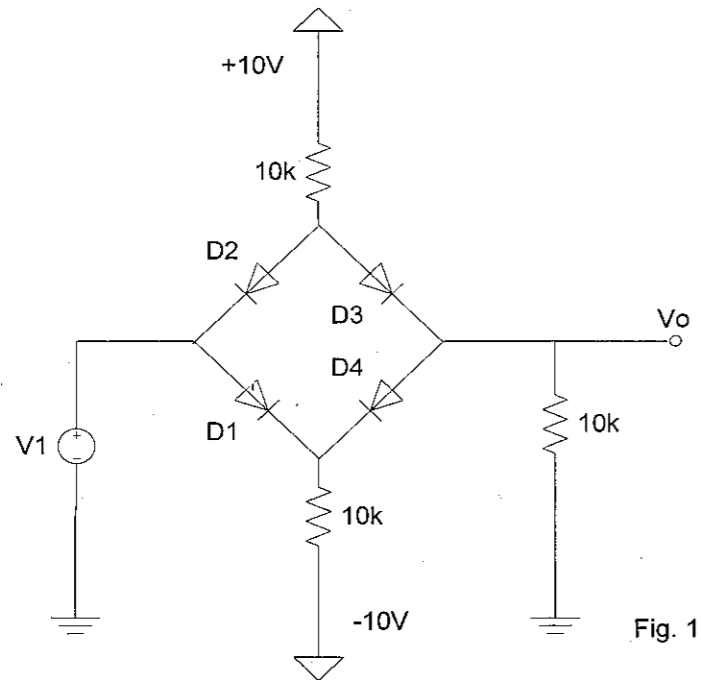


Fig. 1

二、The triangle wave generator shown in Fig. 2. consist of two identical operational amplifiers' whose saturation output voltage can be expressed as  $V_{sat} = (\text{supply voltage}) - 1.5 = 15 - 1.5 = 13.5 \text{ V}$ .

1. Find the waveforms of the output voltages  $V_{o1}$  and  $V_{o2}$ , if switch  $S_1$  is kept closed and switch  $S_2$  open. Draw the waveforms to the same horizontal time-scale. Determine the positive negative peak values and the frequency for  $V_{o2}$  (10 分)
2. Repeat(1), if  $S_1$  is kept open while  $S_2$  closed. (10 分)


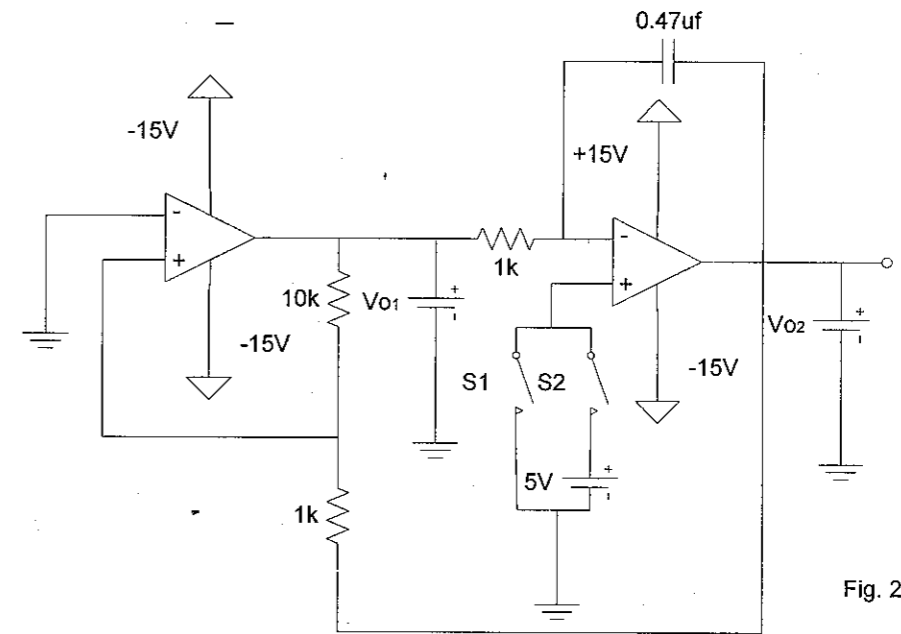


Fig. 2


注意：背面尚有試題

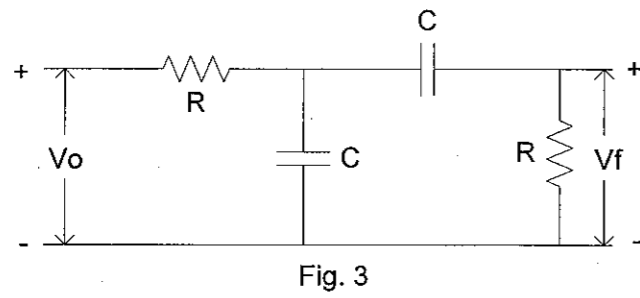- 三、1. For the feedback network shown in Fig. 3 find the transfer function  $V_f/V_o$ . (6分)
2. This network is used with an AMP to form an oscillator. Find the frequency of oscillation and the minimum amplifier gain. (7分)
3. Draw the network connected to the OP AMP to form oscillator. (7分)



- 四、An active RC Band-pass filter as shown, verify  $\frac{V_o(s)}{V_s(s)} = \frac{-S/R_1C}{S^2 + \left(\frac{2}{R_3C}\right)S + \frac{1}{R'R_3C^2}}$

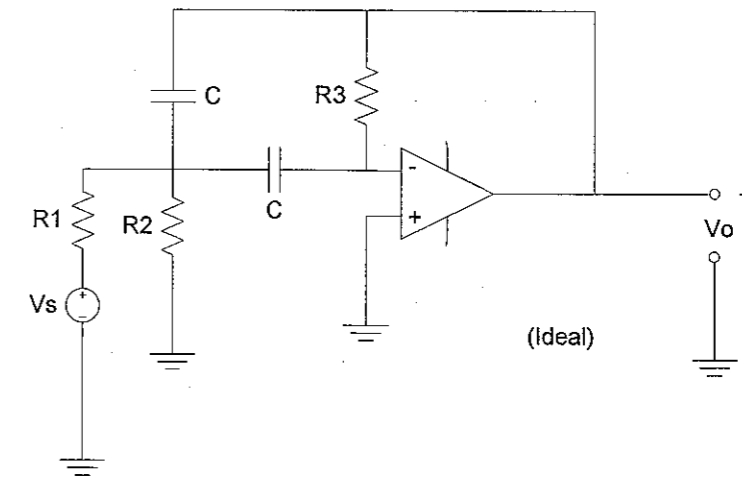where  $R' = \frac{R_1R_2}{R_1 + R_2}$  (20分)



五、For the circuit shown below, find  $Z_{in} = ?$  (20 分)

