

國立臺北科技大學九十八學年度碩士班招生考試

系所組別：2111 電機工程系碩士班甲組

第一節 電力系統 試題

第一頁 共一頁

注意事項：

1. 本試題共五題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

一、(35%) Briefly explain the following questions:

1. What are the differences between the long distance and short distance transmission line models? (5%)
2. What are the functions of a distance relay? (5%)
3. What are the meanings of the swing equation? (5%)
4. How does a power plant control its output real power? (4%)
5. How does a synchronous generator control its output reactive power? (4%)
6. How does an induction generator control its output reactive power? (4%)
7. What are the functions of a Capacitive Voltage Transformer (CVT)? (4%)
8. What are the meanings of the PV bus? (4%)

二、(16%) A 22kV three-phase Y-connected 500MVA synchronous generator has 0.1pu synchronous reactance on each phase.

1. Find the real Ohm value of the synchronous reactance (8%)
2. If the S_{base} is changed to 400MVA and the V_{base} is changed to 20kV, find the new per-unit value of the synchronous reactance. (8%)

三、(16%) In fig.1, two ideal voltage sources V_1 and V_2 are connected by an impedance Z .

1. Which voltage source consumes the real power? What is the value of the consumed real power? (8%)
2. Which voltage source generates the reactive power? What is the value of the generated reactive power? (8%)

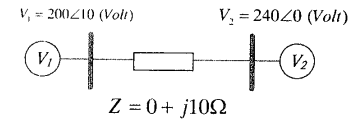


Fig.1

四、(15%) In fig.2, an unbalanced three-phase Δ -connected voltage sources

$$(V_{ab} = 100\angle 0^\circ \text{ (Volt)}, V_{bc} = 80\angle -121^\circ \text{ (Volt)}, V_{ca} = 110\angle 130^\circ \text{ (Volt)})$$

is connected with a balanced Y-connected 10Ω three-phase load

1. Obtain the symmetric component of the line voltage. (5%)
2. Obtain the real power consumed in positive sequence network. (5%)
3. Obtain the real power consumed in negative sequence network. (5%)

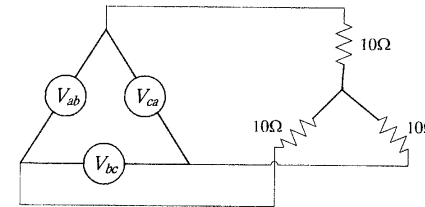


Fig.2

五、(18%) In fig.3, a system with two generators and one load has been economic dispatched.

Find the generation power P_{G1} , P_{G2} and the load power P_D , when the dispatched λ

(Lagrange multiplier) is \$6/Mwh.

$$IC_1 = 0.007P_{G1} + 4.1 \$ / Mwh$$

$$IC_2 = 0.007P_{G2} + 4.1 \$ / Mwh,$$

IC : Incremental cost, P_L : Line loss

$$P_L = 0.01P_{G2}^2$$

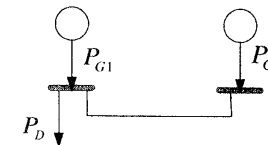


Fig.3

Handwritten note: Z_{0-1}