

國立臺北科技大學九十九學年度碩士班招生考試

系所組別：2401 光電工程系碩士班

第三節 電子學 試題 (選考)

第一頁 共二頁

注意事項：

1. 本試題共 6 題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

1. Consider a full-wave bridge rectifier circuit, as shown in Fig.1, to design a dc power supply that provides an average dc output voltage of 15 V on which a maximum of ± 1 V ripple is allowed. The rectifier has a load of resistance $R=150\Omega$. The rectifier is fed from the line voltage 120 V, 60 Hz through a transformer. The diodes available have 0.7-V drop when conducting.

- (a) Find the required value of the filter capacitor C . (5%)
- (b) Find the maximum reverse voltage that will appear across the diode. (5%)
- (c) Calculate the average current through the diode during conduction. (5%)

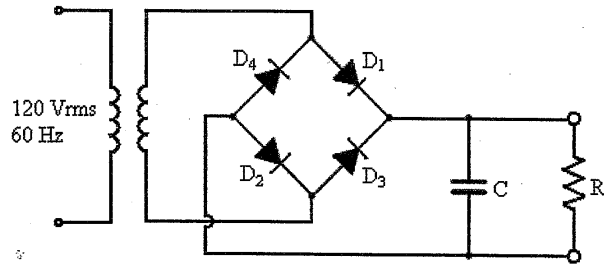


Fig. 1

2. For the circuit in Fig. 2, find the base voltage V_B and the emitter voltage V_E of the transistors Q_1 and Q_2 when the input voltage v_i equals to (a) +3 V (b) -5 V and (c) -10 V. The BJTs have current gain $\beta=100$ when they are biased in active mode. (15% ; each 5%)

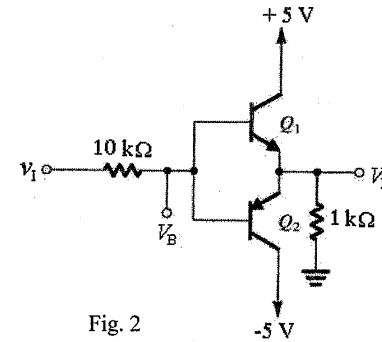


Fig. 2

3. In Fig. 3, consider a three-stage amplifier in which the stages are directly coupled. Assume that the capacitors are large enough to act as perfect short circuits at all signal frequencies of interest.
 - (a) Consider the dc bias current in each of the three transistors and then find the dc voltage at the output. Assume the base to emitter voltage $|V_{BE}|=0.7$ V and current gain $\beta=100$ for the BJTs biased in active mode, and neglect the Early effect. (5%)
 - (b) Find the input resistance and the output resistance. (5%)
 - (c) Use the current-gain method to find the voltage gain v_o / v_i . (5%)
 - (d) Find the frequency of the high-frequency pole formed at the interface between the first and the second stages. Assume that $C_{\mu 2}=2$ pF and $C_{\pi 2}=10$ pF. (5%)

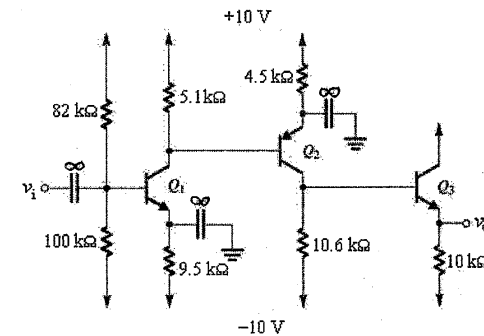


Fig. 3

注意：背面尚有試題

4. For the shunt-series feedback amplifier of Fig. 4, derive expressions for current gain $A_f = I_o/I_s$ and input resistance R_{in} . Neglect r_o and the body effect. (15%)

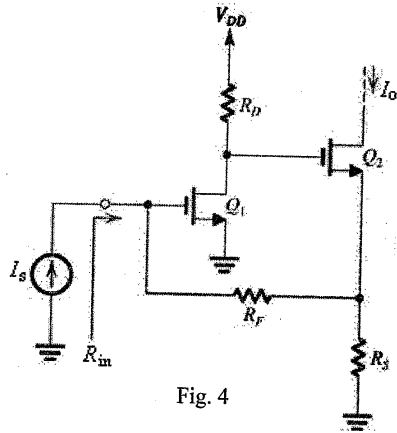


Fig. 4

6. Consider the circuit in Fig. 6. (a) Break the feedback loop at node X and find the loop gain $A\beta = V_o(j\omega)/V_x(j\omega)$. (b) Find the minimum value R_f for oscillation to start. (c) Find the frequency of oscillation f_o . (15%; each 5%)

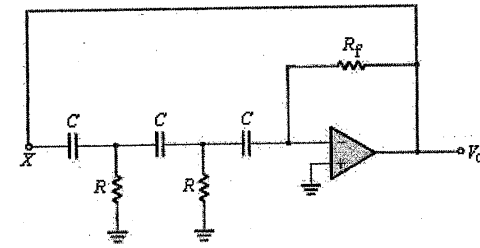


Fig. 6

5. The differential amplifier circuit of Fig. 5 utilizes a resistor connected to the negative power supply to establish the bias current I .
- For $v_{B1} = v_{id}/2$ and $v_{B2} = -v_{id}/2$, where v_{id} is a small signal with zero average, find the magnitude of the differential gain, $|v_o/v_{id}|$. (5%)
 - For $v_{B1} = v_{B2} = v_{icm}$, find the magnitude of the common-mode gain, $|v_o/v_{icm}|$. (5%)
 - Calculate the CMRR. (5%)
 - If $v_{B1} = 0.1 \sin 2\pi \times 60t + 0.005 \sin 2\pi \times 1000t$ volt and $v_{B2} = 0.1 \sin 2\pi \times 60t - 0.005 \sin 2\pi \times 1000t$ volt, find v_o . (5%)

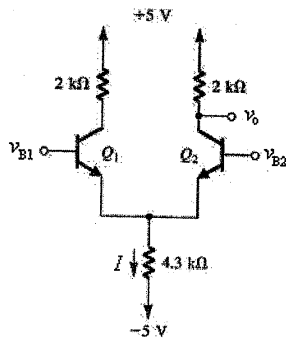


Fig. 5