

國立臺北科技大學九十九學年度碩士班招生考試

系所組別：2240 電腦與通訊研究所丁組

第二節 電子學 試題

第一頁 共二頁

注意事項：

1. 本試題共五題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

一、(20%) Consider the single op-amp difference amplifier in Fig. 1.

1. Please derive the expression for v_o as a function of v_{i1} and v_{i2} . (5%)
2. Please derive the common-mode gain A_{cm} . (10%)
3. Please give the condition using R_1 , R_2 , R_3 , and R_4 to satisfy $CMRR=\infty$. (5%)

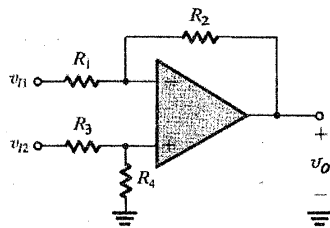


Fig. 1

二、(20%) Consider a common-source amplifier in Fig. 2. Assume the transistor has $V_T=1.5V$, $k'_n(W/L)=0.25mA/V^2$, and $V_A=50V$. The channel-length modulation is neglected.

1. Determine the output resistance r_o . (5%)
2. Determine the small-signal voltage gain A_v . (5%)
3. Determine the input resistance R_{in} . (5%)
4. Determine the maximum allowable input signal peak. (5%)

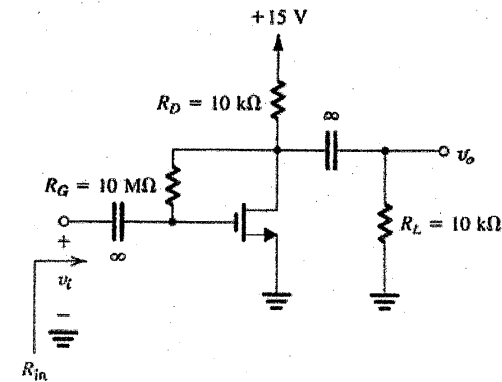


Fig. 2

三、(20%) Consider a current-steering circuit in Fig. 3. Assume the $V_{DD}=V_{SS}=1.5V$, $V_{tn}=0.6V$, $V_{tp}=-0.6V$, all channel lengths= $1\mu m$, $k'_n=200\mu A/V^2$, $k'_p=80\mu A/V^2$, and $\lambda=0$. The $I_{REF}=10\mu A$, $I_2=60\mu A$, $I_3=20\mu A$, and $I_5=80\mu A$. It is further required that the voltage at the drain of Q_2 be allowed to go down to within 0.2V of the negative supply and that the voltage at the drain of Q_5 be allowed to go up to within 0.2V of the positive supply. Please find the widths of all transistors W_1 , W_2 , W_3 , W_4 , and W_5 .

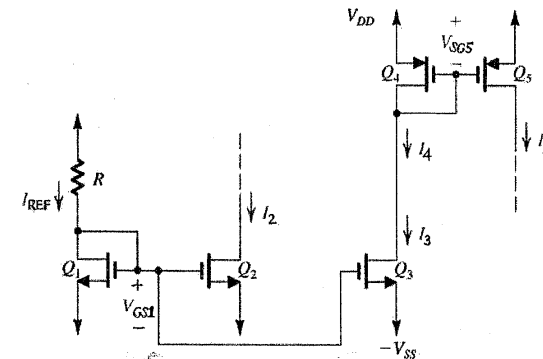


Fig. 3

注意：背面尚有試題

四、(20%) Fig.4 shows an ideal voltage amplifier having a gain of -100 V/V with an impedance Z connected between the output and input terminals.

1. Find the Miller equivalent circuit when Z is $1\text{-M}\Omega$ resistance, and determine V_o/V_{sig} (10%)
2. Find the Miller equivalent circuit when Z is 1-pF capacitance, and determine V_o/V_{sig} (10%)

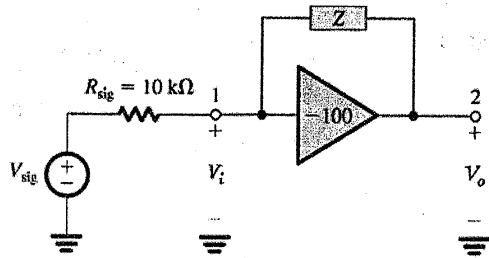


Fig. 4

五、(20%) Fig.5 shows an active-load bipolar differential pair.

1. Assume the input signals $v_{B1} = +v_{id}/2$ and $v_{B2} = -v_{id}/2$. Please plot the small-signal equivalent circuit and to determine the overall short-circuit transconductance $G_m \equiv i_o/v_{id}$. (10%)
2. Please plot the equivalent circuit and to determine the output resistance R_o . (10%)

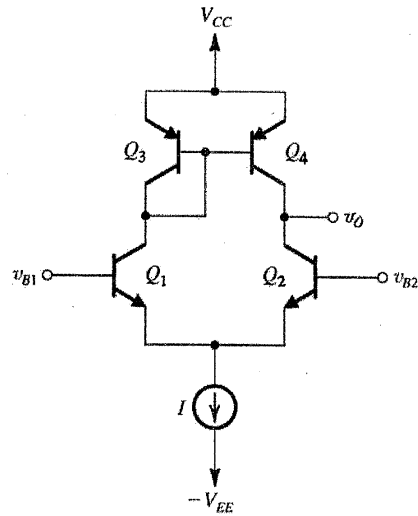


Fig. 5